



# *Digital Integrated Circuits*

## *A Design Perspective*

Jan M. Rabaey  
Anantha Chandrakasan  
Borivoje Nikolic

# Semiconductor Memories

*December 20, 2002*


# *Chapter Overview*

- ☐ **Memory Classification**
- ☐ **Memory Architectures**
- ☐ **The Memory Core**
- ☐ **Periphery**
- ☐ **Reliability**
- ☐ **Case Studies**


# *Semiconductor Memory Classification*

Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM E <sup>2</sup> PROM FLASH	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CAM		


# Memory Timing: Definitions

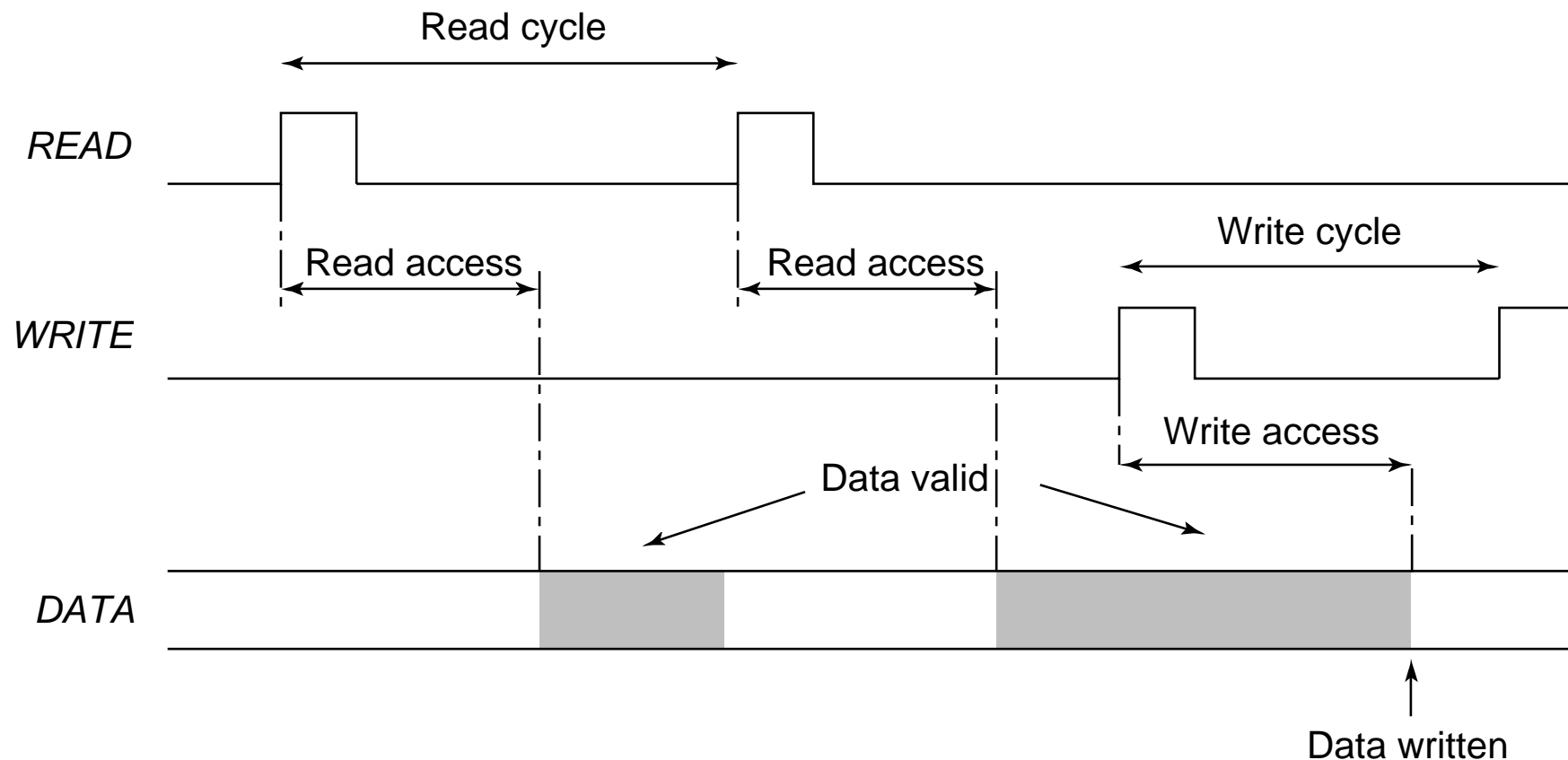

# Memory Architecture: Decoders

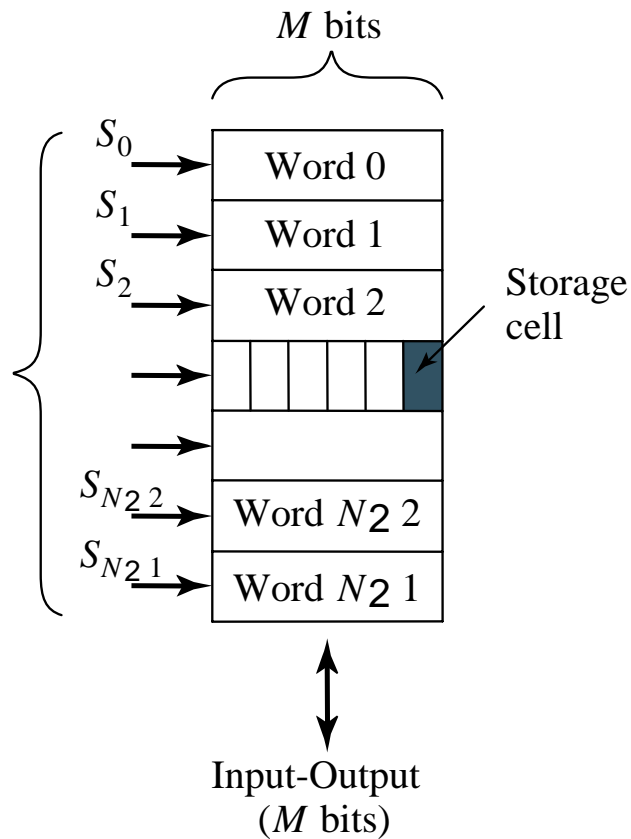

 
Intuitive architecture for  $N \times M$  memory  
 Too many select signals:  
 $N$  words ==  $N$  select signals




Decoder reduces the number of select signals  
 $K = \log_2 N$

# Array-Structured Memory Architecture

 **Problem: ASPECT RATIO or HEIGHT >> WIDTH**




# Hierarchical Memory Architecture

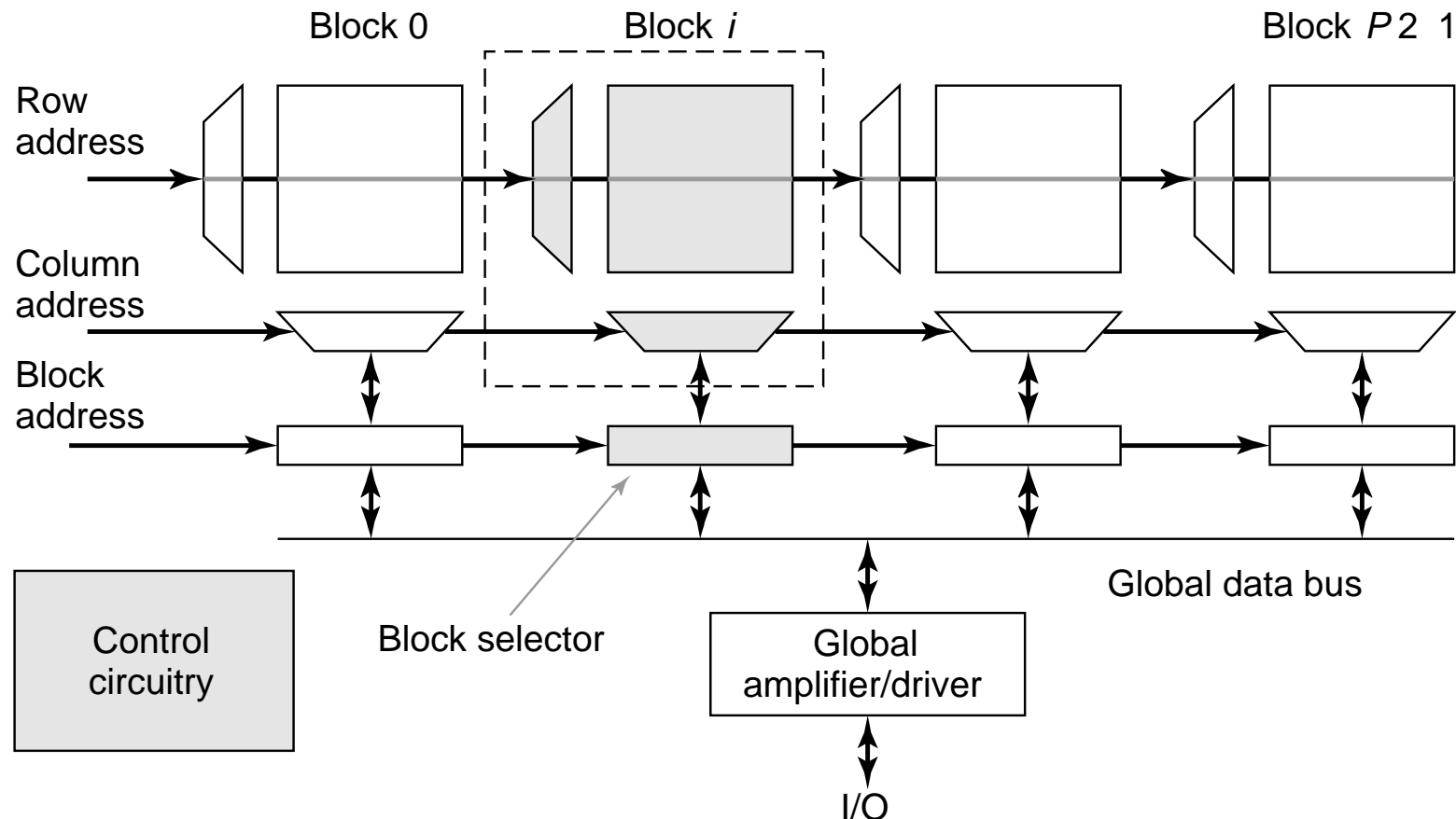

## Advantages:


1. Shorter wires within blocks
2. Block address activates only 1 block => power savings

# Block Diagram of 4 Mbit SRAM

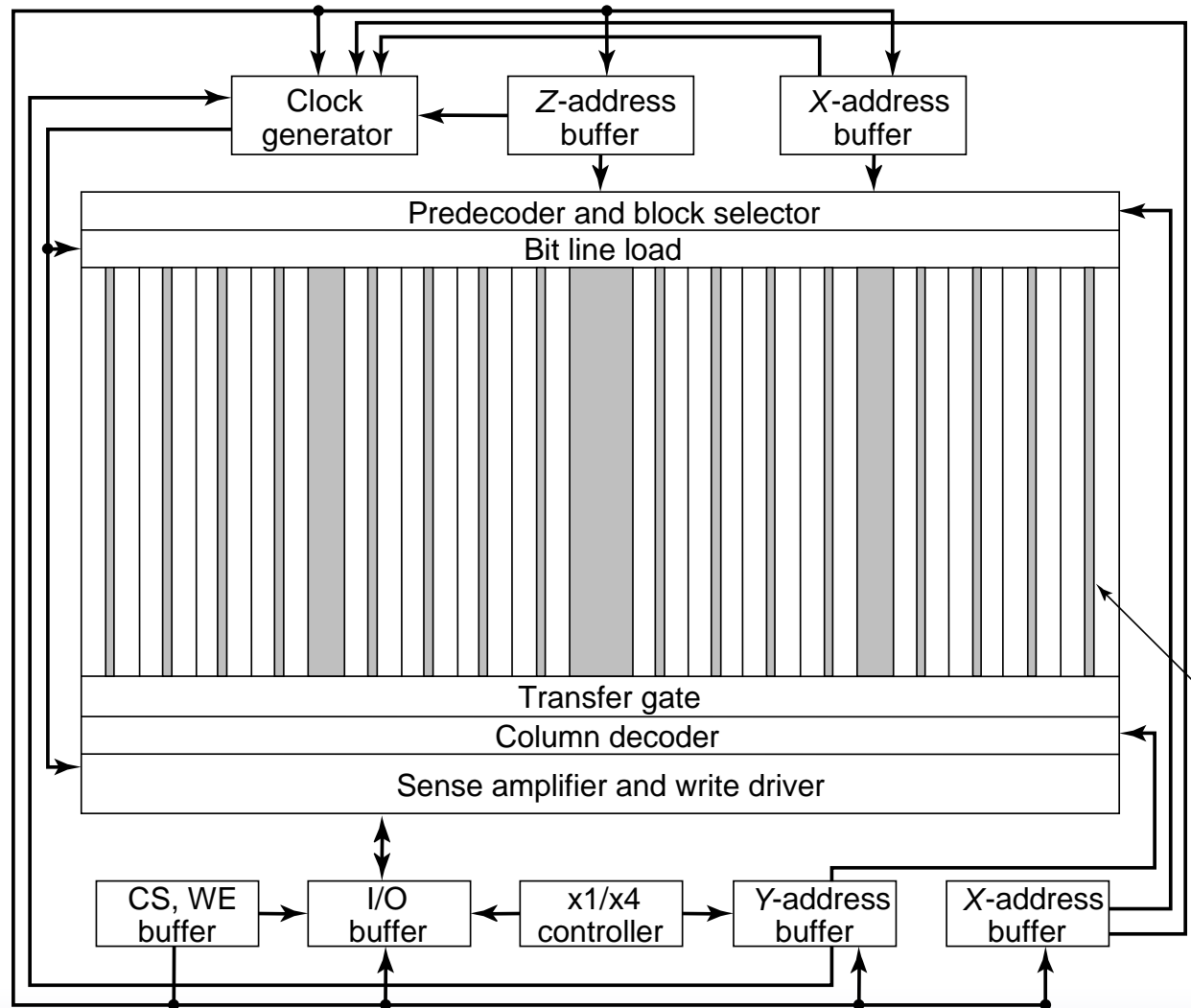





# Contents-Addressable Memory

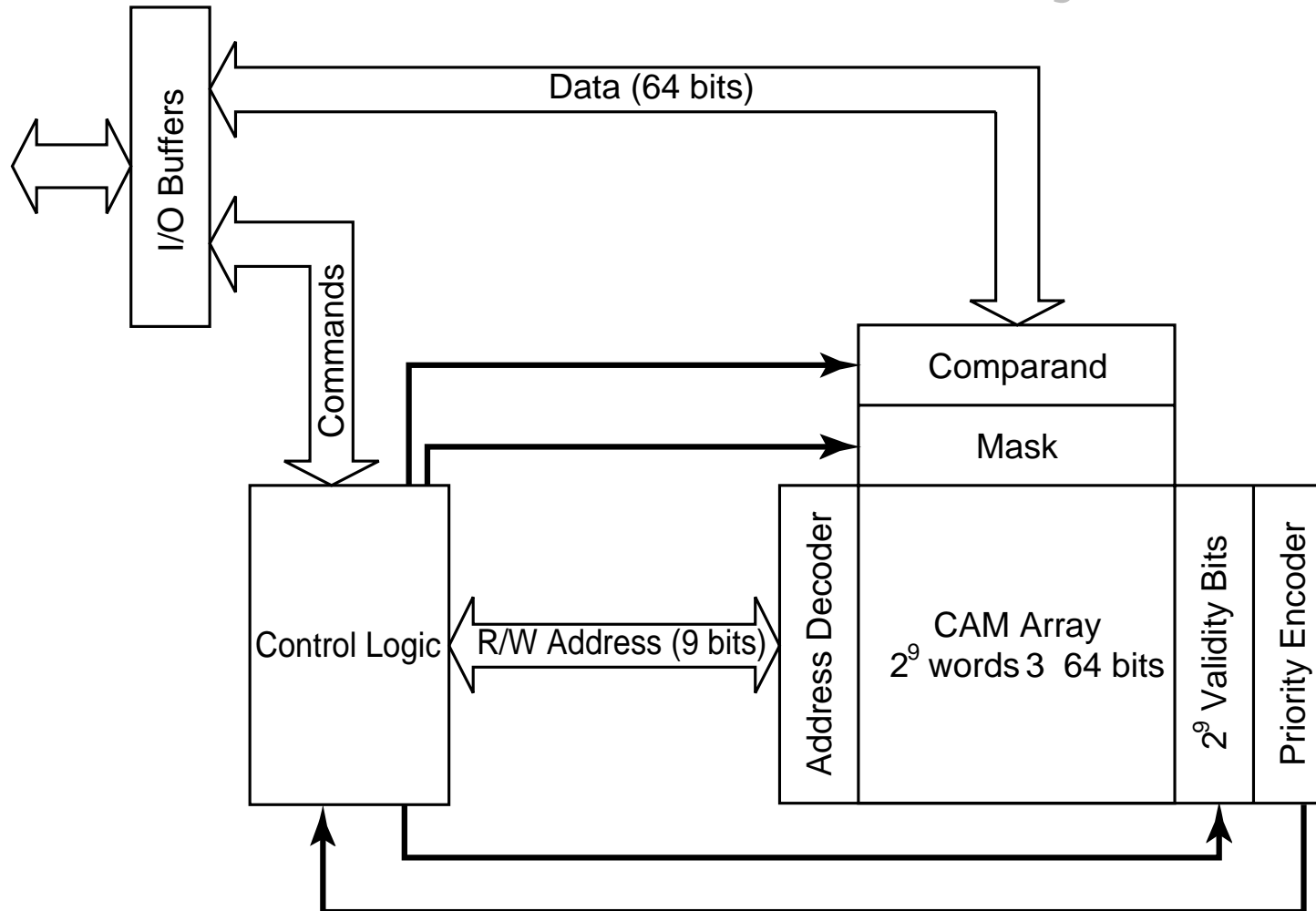

# Memory Timing: Approaches

 


 **DRAM Timing**  
**Multiplexed Addressing**




**SRAM Timing**  
**Self-timed**


# Read-Only Memory Cells

 




Diode ROM

 


MOS ROM 1

 


MOS ROM 2

   


# MOS OR ROM

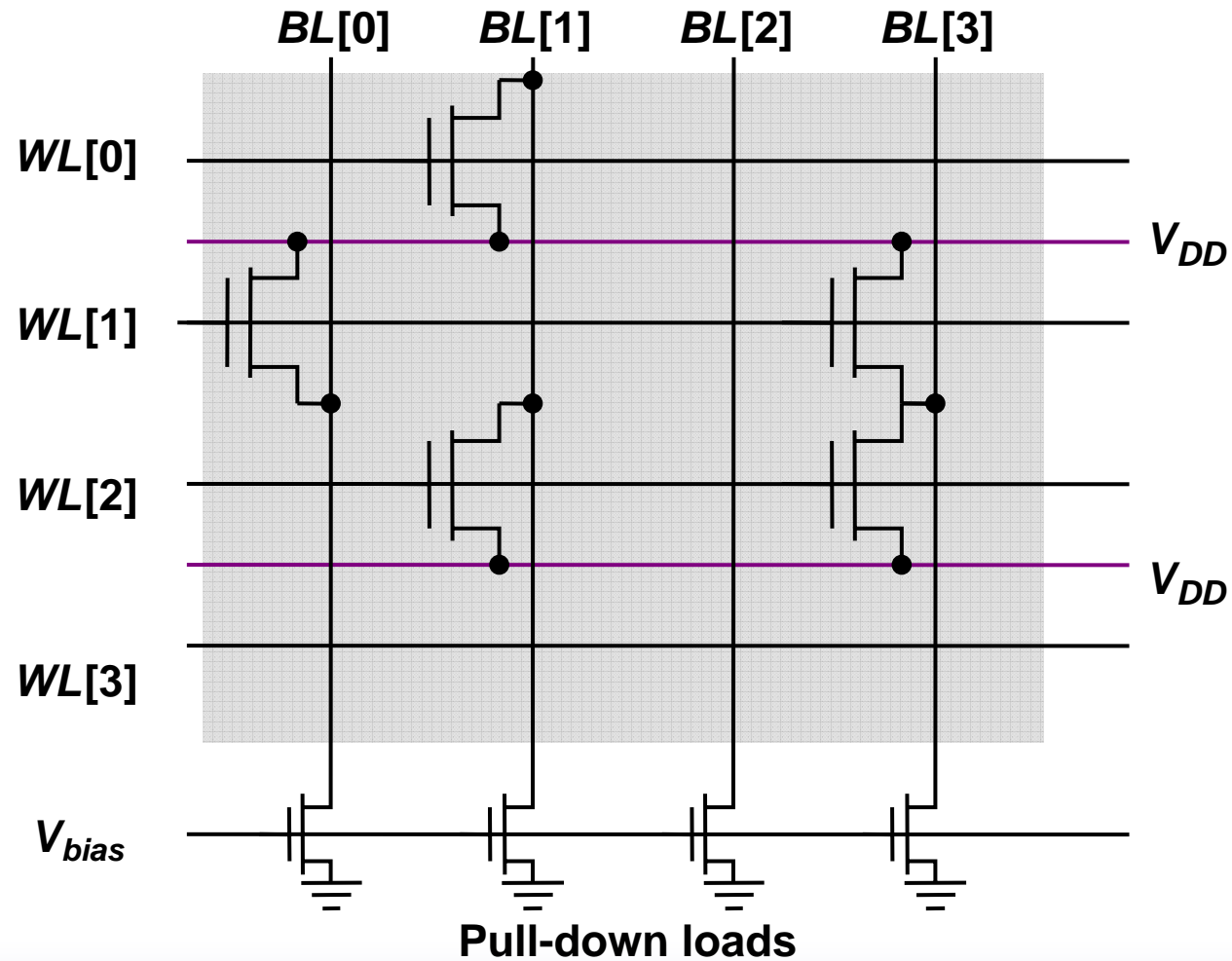

# MOS NOR ROM

 

 
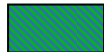


# MOS NOR ROM Layout




Cell ( $9.5\lambda \times 7\lambda$ )

**Programmming using the  
Active Layer Only**




-  Polysilicon
-  Metal1
-  Diffusion
-  Metal1 on Diffusion

# MOS NOR ROM Layout

 
Cell ( $11\lambda \times 7\lambda$ )



**Programmming using  
the Contact Layer Only**

-  Polysilicon
-  Metal1
-  Diffusion
-  Metal1 on Diffusion


# MOS NAND ROM

 

 All word lines high by default with exception of selected row






# MOS NAND ROM Layout



Cell ( $8\lambda \times 7\lambda$ )


**Programmming using  
the Metal-1 Layer Only**

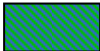No contact to VDD or GND necessary;  
drastically reduced cell size  
Loss in performance compared to NOR ROM




-  Polysilicon
-  Diffusion
-  Metal1 on Diffusion

# NAND ROM Layout

 
Cell ( $5\lambda \times 6\lambda$ )




**Programmming using  
Implants Only**

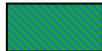-  Polysilicon
-  Threshold-altering implant
-  Metal1 on Diffusion

# Decreasing Word Line Delay

 

 
(a) Driving the word line from both sides



(b) Using a metal bypass

(c) Use silicides


# Precharged MOS NOR ROM

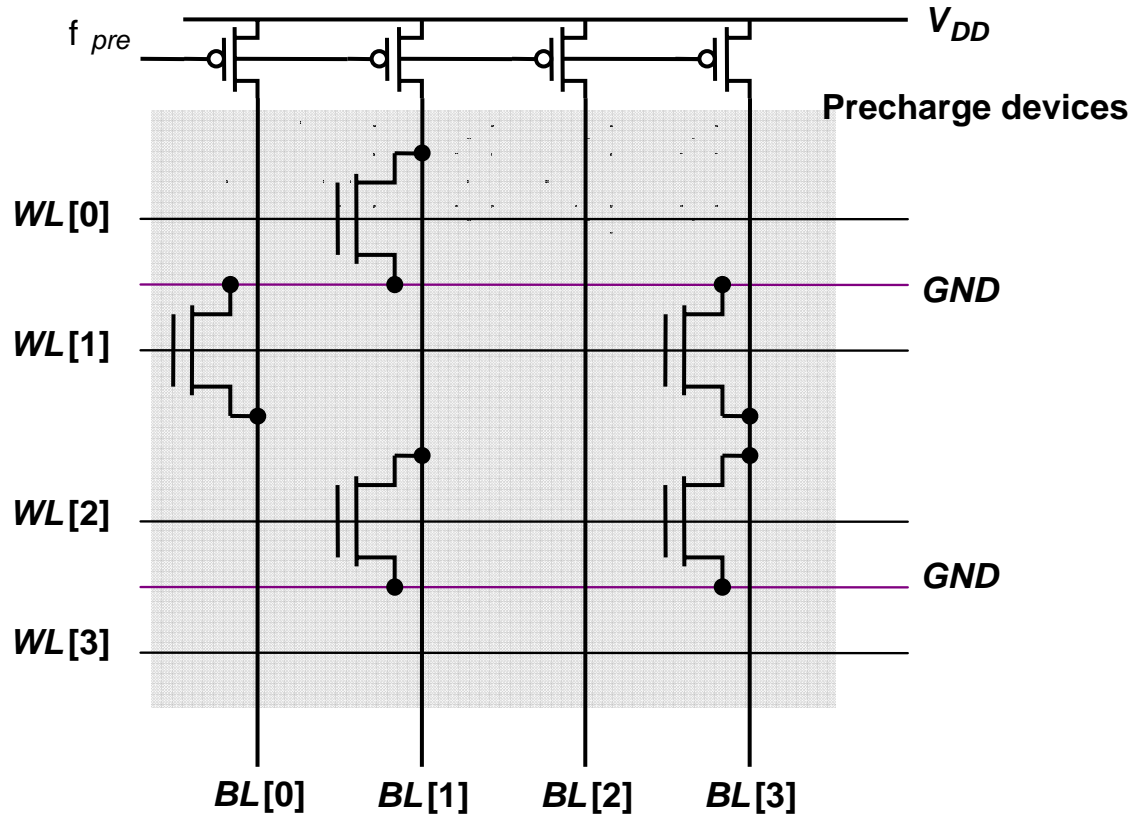


**PMOS precharge device can be made as large as necessary, but clock driver becomes harder to design.**

# *Non-Volatile Memories*
 
## *The Floating-gate transistor (FAMOS)*




Device cross-section

 


Schematic symbol


# Floating-Gate Transistor Programming

 

**Avalanche injection**

 


 **Removing programming voltage leaves charge trapped**




**Programming results in higher  $V_T$ .**


# A “Programmable-Threshold” Transistor

 

# ***FLOTOX EEPROM***

 


**FLOTOX transistor**

 

**Fowler-Nordheim  
 $I$ - $V$  characteristic**



# EEPROM Cell

 


**Absolute threshold control  
is hard**

**Unprogrammed transistor  
might be depletion**


⇒ **2 transistor cell**

# Flash EEPROM

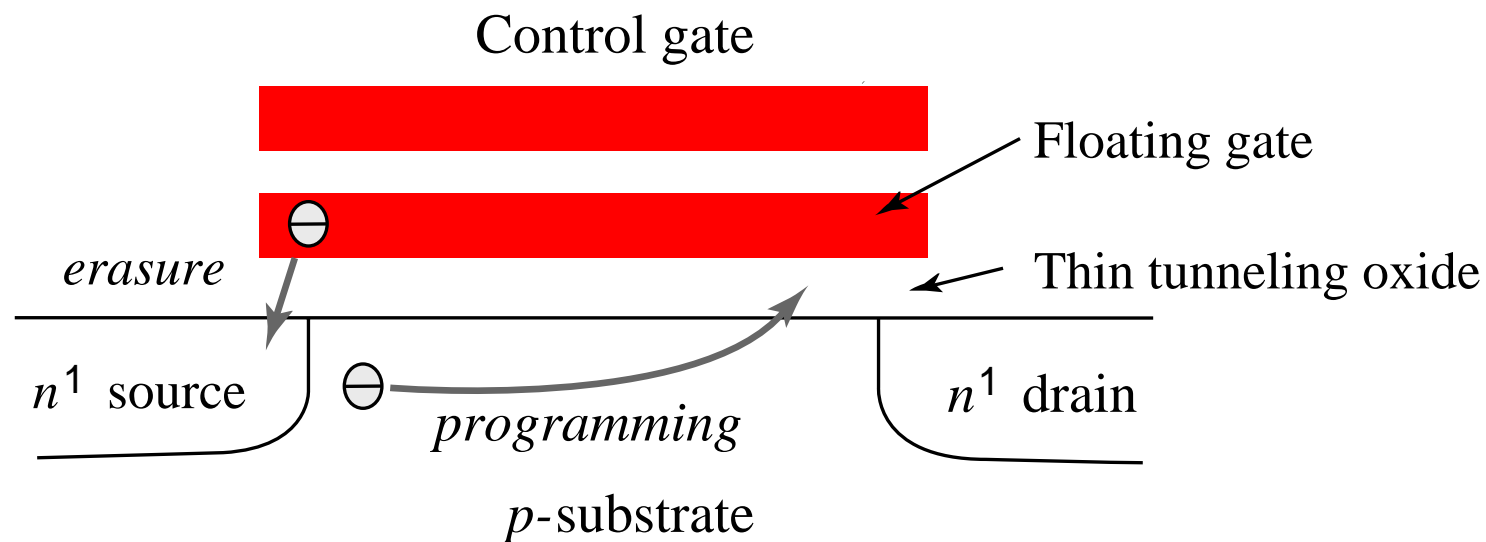

**Many other options ...**



# Cross-sections of NVM cells

 



**Flash**

**EPROM**

  
# Basic Operations in a NOR Flash Memory— Erase



 
 
# Basic Operations in a NOR Flash Memory— Write



 
# Basic Operations in a NOR Flash Memory— Read



# NAND Flash Memory

 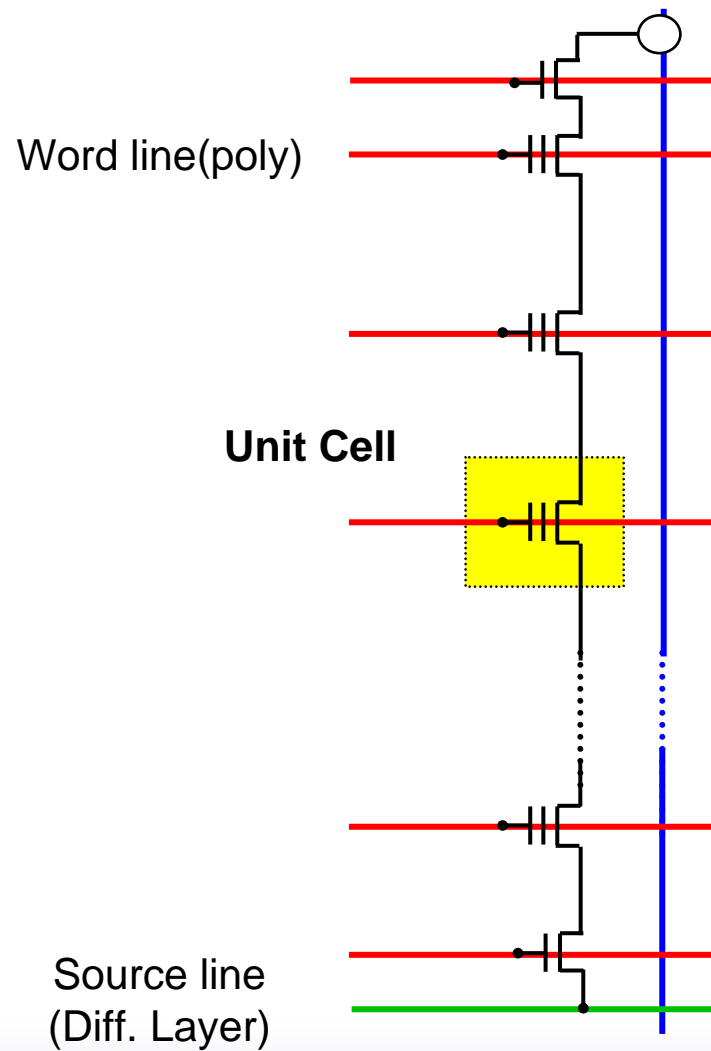

# *NAND Flash Memory*

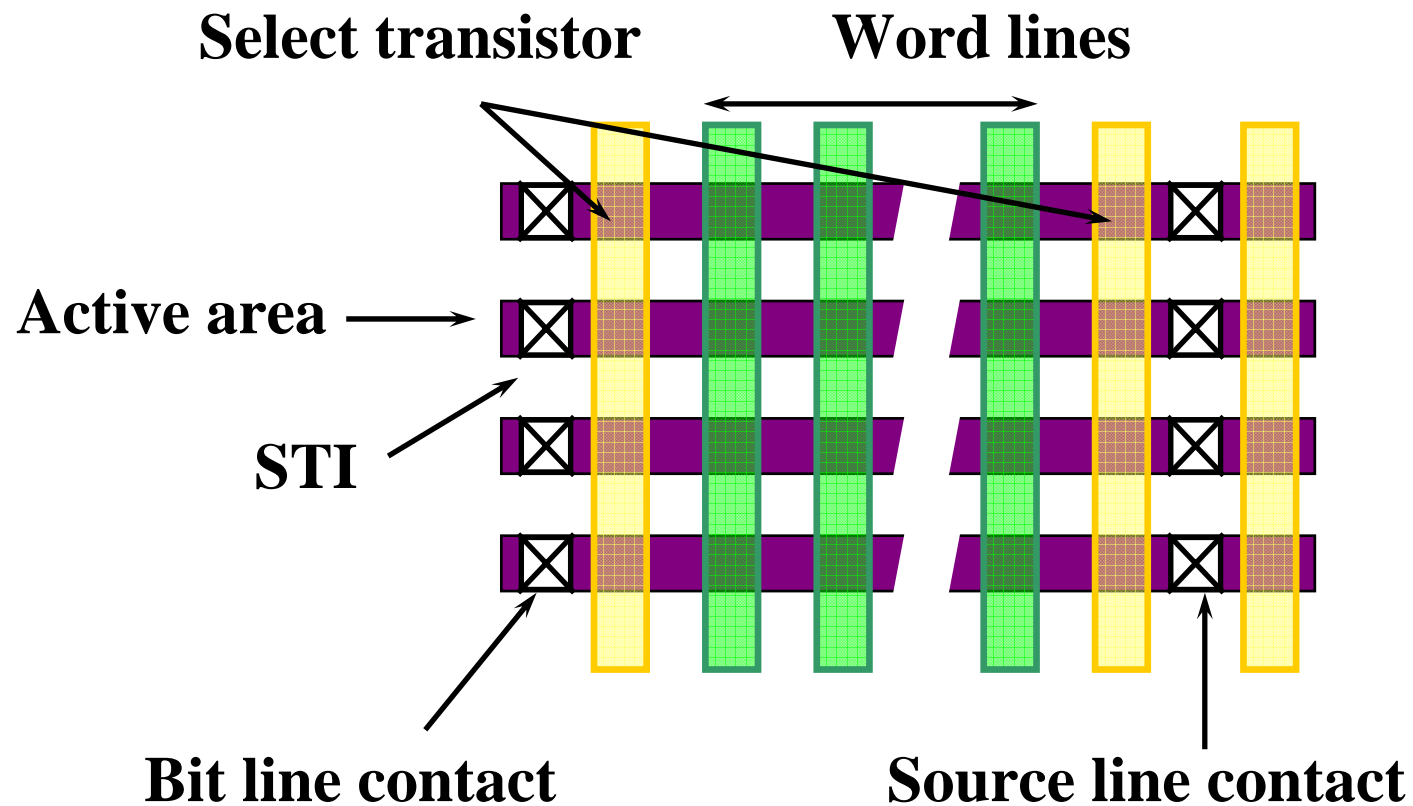



# Characteristics of State-of-the-art NVM

**Table 12-1** Comparison between nonvolatile memories ([Itoh01]).

$V_{DD} = 3.3$  or  $5$  V;  $V_{PP} = 12$  or  $12.5$  V.

	Cell— Nr. of Transistors	Cell Area (ratio wrt EPROM)	Mechanism		External Power Supply		Program/ Erase Cycles
			Erase	Write	Write	Read	
MASK ROM	1 T (NAND)	0.35–5	—	—	—	$V_{DD}$	0
EPROM	1 T	1	UV Exposure	Hot electrons	$V_{PP}$	$V_{DD}$	~100
EEPROM	2 T	3–5	FN Tunneling	FN Tunneling	$V_{PP}$ (int)	$V_{DD}$	$10^4$ – $10^5$
Flash Memory	1 T	1–2	FN Tunneling	Hot electrons	$V_{PP}$	$V_{DD}$	$10^4$ – $10^5$
			FN Tunneling	FN Tunneling	$V_{PP}$ (int)	$V_{DD}$	$10^4$ – $10^5$

# ***Read-Write Memories (RAM)***

## **❑ STATIC (SRAM)**

**Data stored as long as supply is applied**

**Large (6 transistors/cell)**

**Fast**

**Differential**

## **❑ DYNAMIC (DRAM)**


**Periodic refresh required**

**Small (1-3 transistors/cell)**


**Slower**

**Single Ended**

# 6-transistor CMOS SRAM Cell

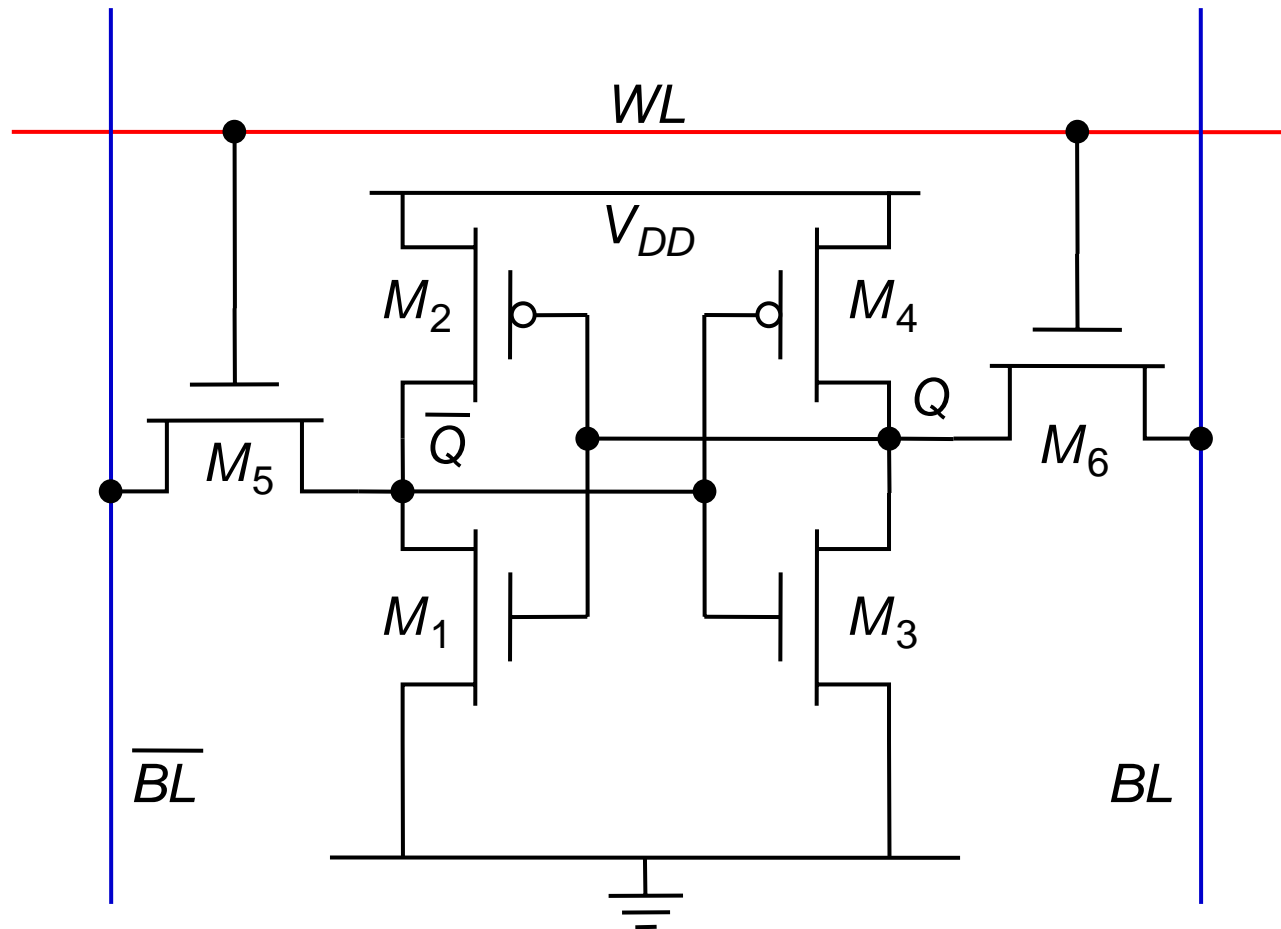


# CMOS SRAM Analysis (Read)

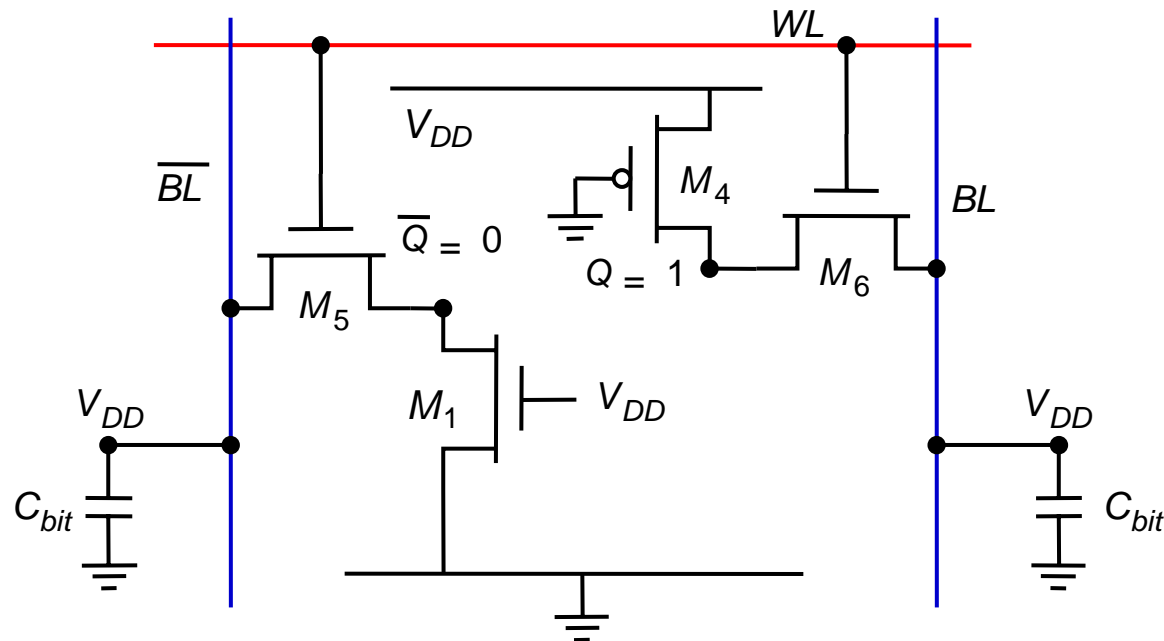

$$k_{n,M5} \left( (V_{DD} - \Delta V - V_{Tn}) V_{DSATn} - \frac{V_{DSATn}^2}{2} \right) = k_{n,M1} \left( (V_{DD} - V_{Tn}) \Delta V - \frac{\Delta V^2}{2} \right)$$


$$\Delta V = \frac{V_{DSATn} + CR(V_{DD} - V_{Tn}) - \sqrt{V_{DSATn}^2(1 + CR) + CR^2(V_{DD} - V_{Tn})^2}}{CR}$$

# CMOS SRAM Analysis (Read)

 

$$CR = \frac{W_1/L_1}{W_5/L_5}$$


# CMOS SRAM Analysis (Write)

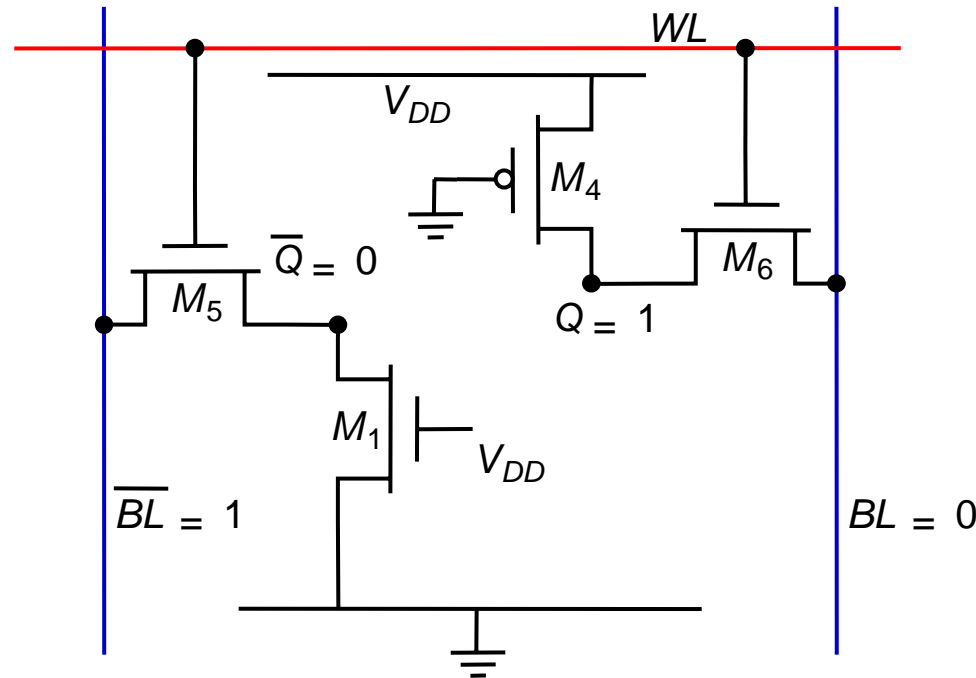


$$k_{n,M6} \left( (V_{DD} - V_{Tn}) V_Q - \frac{V_Q^2}{2} \right) = k_{p,M4} \left( (V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)$$

$$V_Q = V_{DD} - V_{Tn} - \sqrt{(V_{DD} - V_{Tn})^2 - 2 \frac{\mu_p}{\mu_n} PR \left( (V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)},$$

# CMOS SRAM Analysis (Write)

 


# 6T-SRAM — Layout

 



# Resistance-load SRAM Cell

 


Static power dissipation -- Want  $R_L$  large  
Bit lines precharged to  $V_{DD}$  to address  $t_p$  problem

# SRAM Characteristics

**Table 12-2** Comparison of CMOS SRAM cells used in 1-Mbit memory  
(from [Takada91])

	<b>Complementary CMOS</b>	<b>Resistive Load</b>	<b>TFT Cell</b>
Number of transistors	6	4	4 (+2 TFT)
Cell size	58.2 $\mu\text{m}^2$ (0.7- $\mu\text{m}$ rule)	40.8 $\mu\text{m}^2$ (0.7- $\mu\text{m}$ rule)	41.1 $\mu\text{m}^2$ (0.8- $\mu\text{m}$ rule)
Standby current (per cell)	$10^{-15}$ A	$10^{-12}$ A	$10^{-13}$ A

# 3-Transistor DRAM Cell

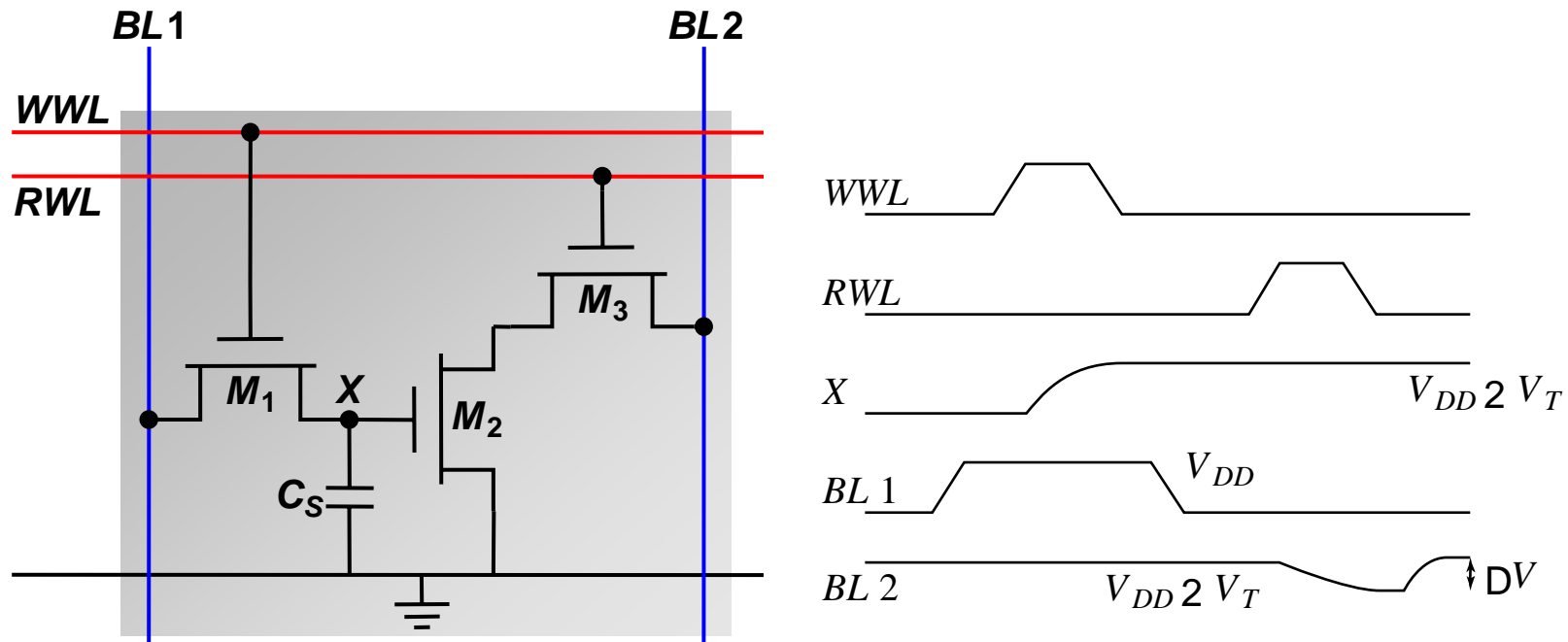


No constraints on device ratios


Reads are non-destructive

Value stored at node X when writing a “1” =  $V_{WWL} - V_{Tn}$

# 3T-DRAM — Layout

 

# 1-Transistor DRAM Cell

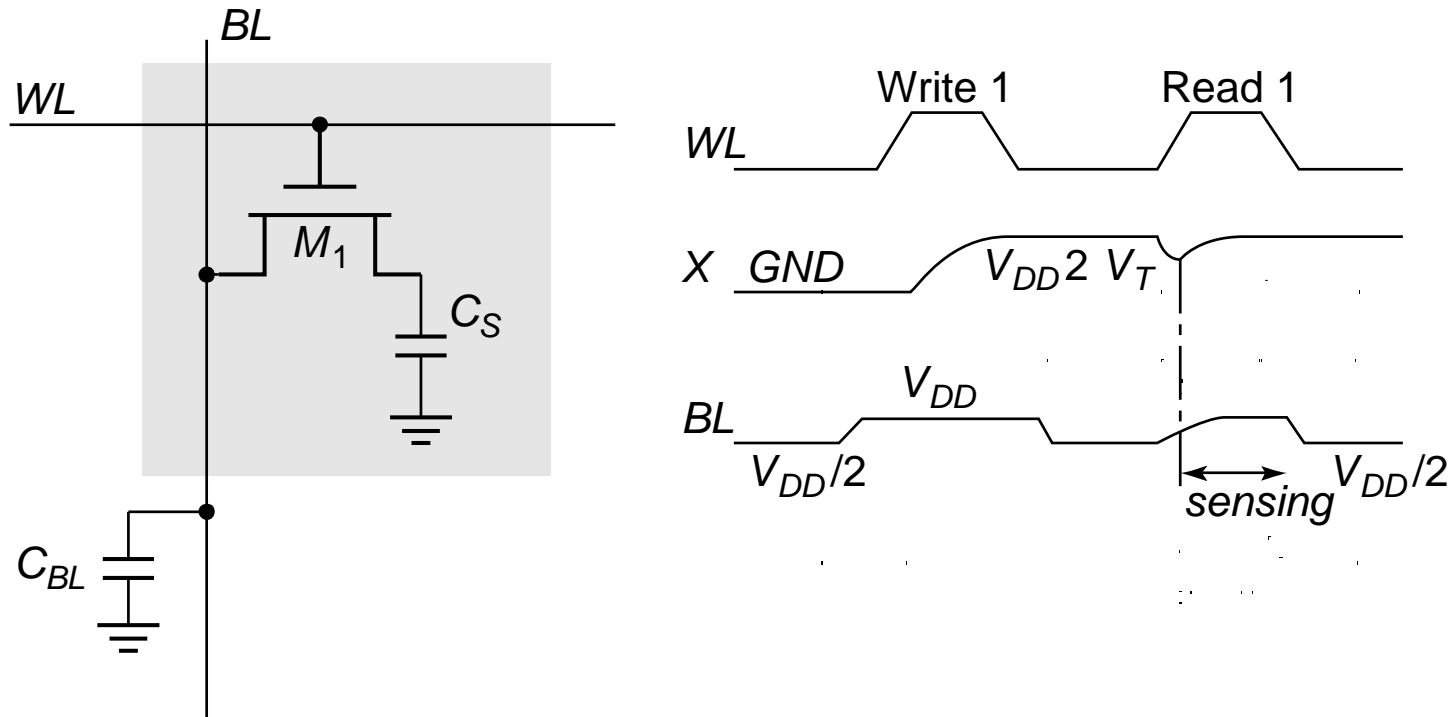

**Write:**  $C_S$  is charged or discharged by asserting WL and BL.

**Read:** Charge redistribution takes places between bit line and storage capacitance


$$\Delta V = V_{BL} - V_{PRE} = V_{BIT} - V_{PRE} \frac{C_S}{C_S + C_{BL}}$$

**Voltage swing is small; typically around 250 mV.**


# ***DRAM Cell Observations***

- ❑ 1T DRAM requires a sense amplifier for each bit line, due to charge redistribution read-out.
- ❑ DRAM memory cells are single ended in contrast to SRAM cells.
- ❑ The read-out of the 1T DRAM cell is destructive; read and refresh operations are necessary for correct operation.
- ❑ Unlike 3T cell, 1T cell requires presence of an extra capacitance that must be explicitly included in the design.
- ❑ When writing a “1” into a DRAM cell, a threshold voltage is lost. This charge loss can be circumvented by bootstrapping the word lines to a higher value than  $V_{DD}$


# Sense Amp Operation

 

# 1-T DRAM Cell

 

**Cross-section**

 


**Layout**


**Uses Polysilicon-Diffusion Capacitance**  
**Expensive in Area**




 
## *SEM of poly-diffusion capacitor 1T-DRAM*



# Advanced 1T DRAM Cells


 


**Trench Cell**

  


**Stacked-capacitor Cell**

# Static CAM Memory Cell

  

# ***CAM in Cache Memory***

 

# *Periphery*

- ☐ **Decoders**
- ☐ **Sense Amplifiers**
- ☐ **Input/Output Buffers**
- ☐ **Control / Timing Circuitry**

# Row Decoders

Collection of  $2^M$  complex logic gates  
Organized in regular and dense fashion

## (N)AND Decoder

$$WL_0 = A_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 A_9$$

$$WL_{511} = \bar{A}_0 \bar{A}_1 \bar{A}_2 \bar{A}_3 \bar{A}_4 \bar{A}_5 \bar{A}_6 \bar{A}_7 \bar{A}_8 \bar{A}_9$$


## NOR Decoder

$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$

$$WL_{511} = \overline{A_0 + \bar{A}_1 + \bar{A}_2 + \bar{A}_3 + \bar{A}_4 + \bar{A}_5 + \bar{A}_6 + \bar{A}_7 + \bar{A}_8 + \bar{A}_9}$$

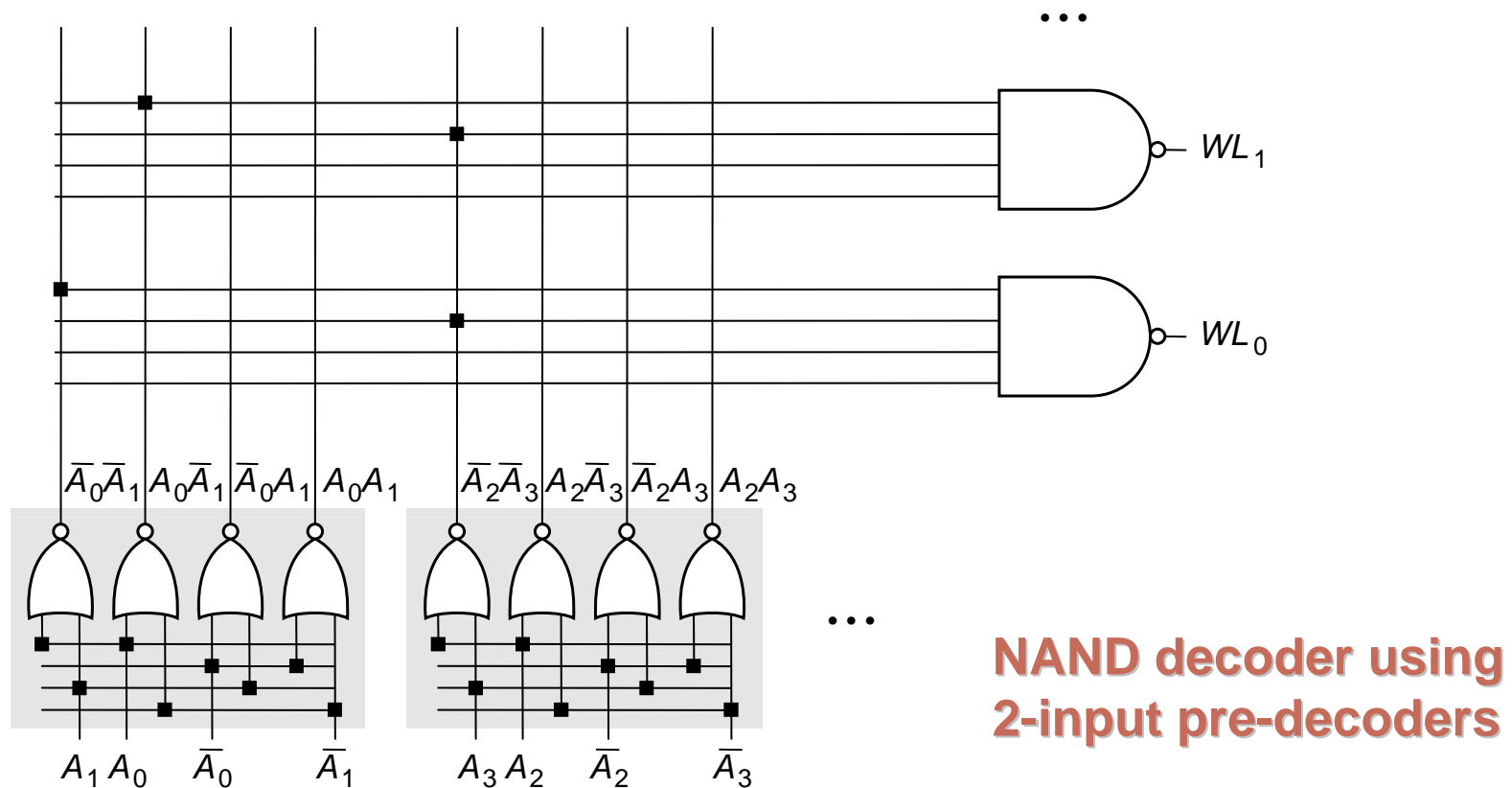
# Hierarchical Decoders

*Multi-stage implementation improves performance*






# Dynamic Decoders

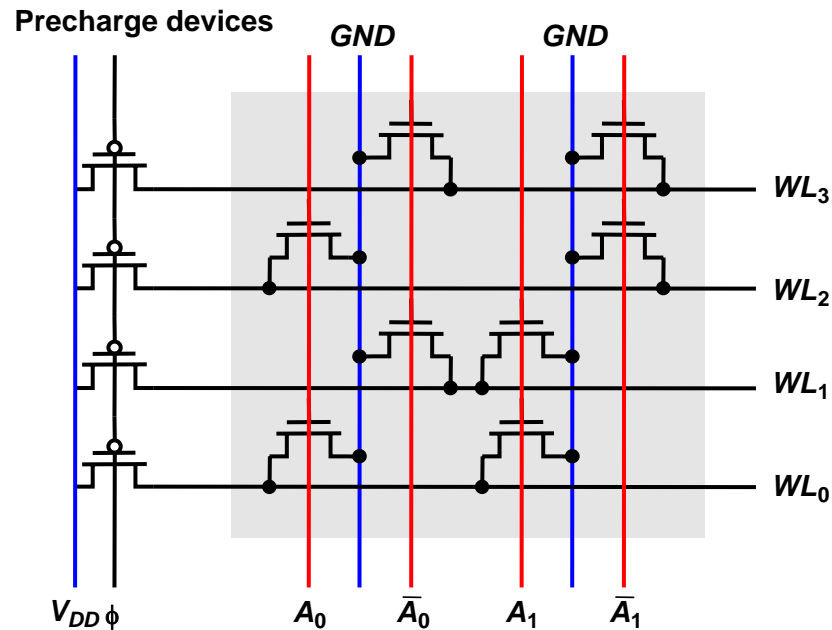


**2-input NOR decoder**

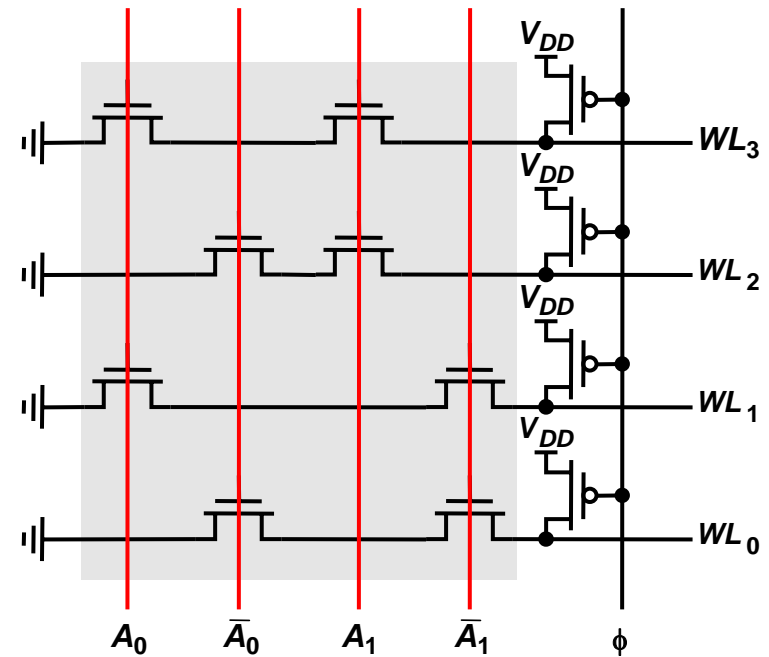

**2-input NAND decoder**


 
## 4-input pass-transistor based column decoder




**Advantages:** speed ( $t_{pd}$  does not add to overall memory access time)

Only one extra transistor in signal path

**Disadvantage:** Large transistor count

# 4-to-1 tree based column decoder

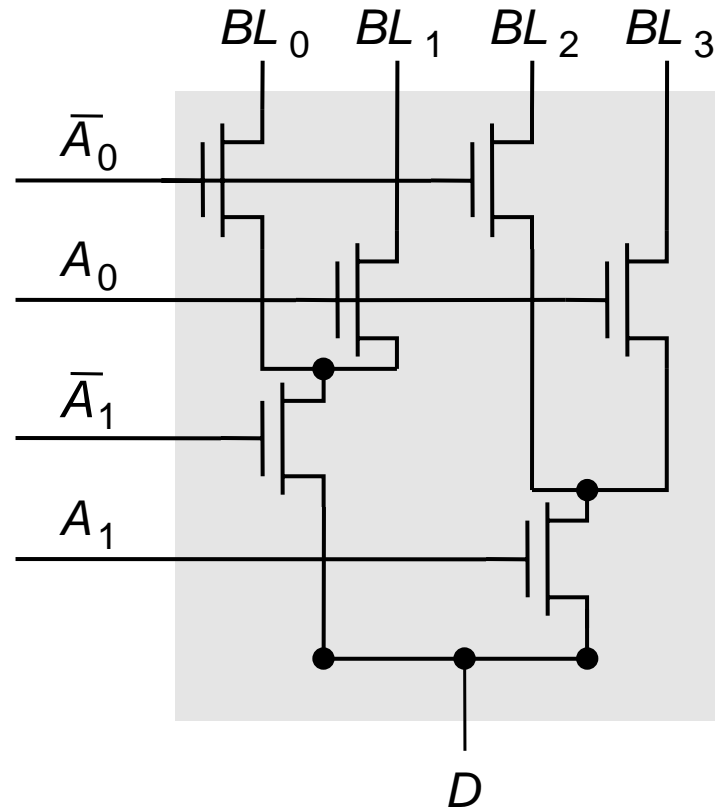

Number of devices drastically reduced


Delay increases quadratically with # of sections; prohibitive for large decoders

Solutions: buffers

progressive sizing

combination of tree and pass transistor approaches

## *Decoder for circular shift-register*

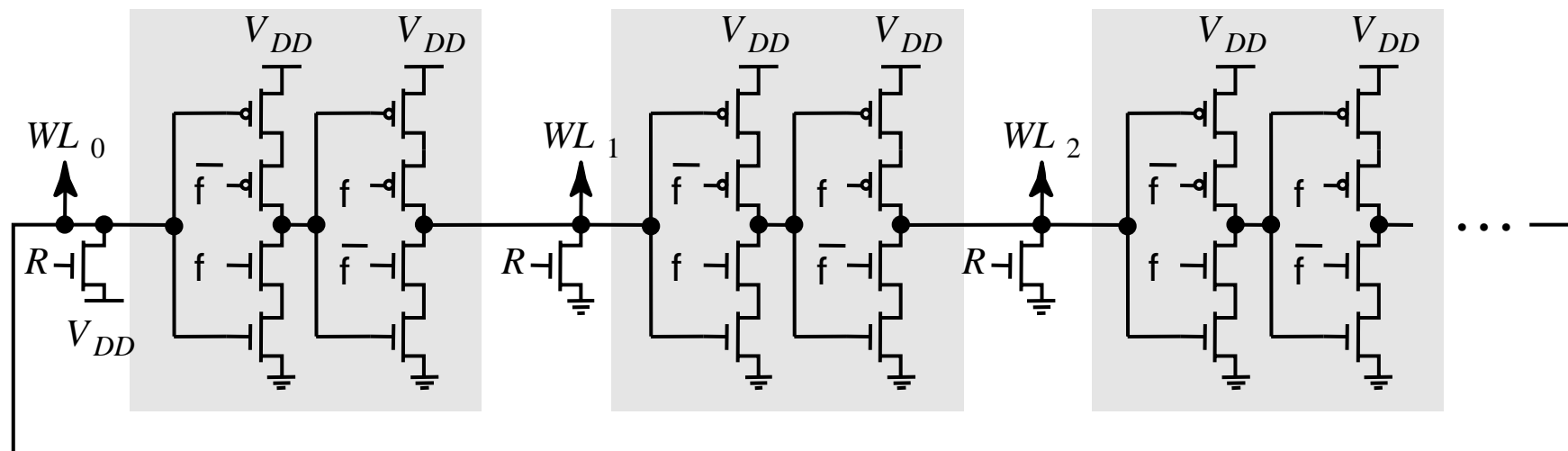

# Sense Amplifiers


$$t_p = \frac{C \cdot \Delta V}{I_{av}}$$

make  $\Delta V$  as small as possible


large

small

**Idea: Use Sense Amplifier**

 


# Differential Sense Amplifier

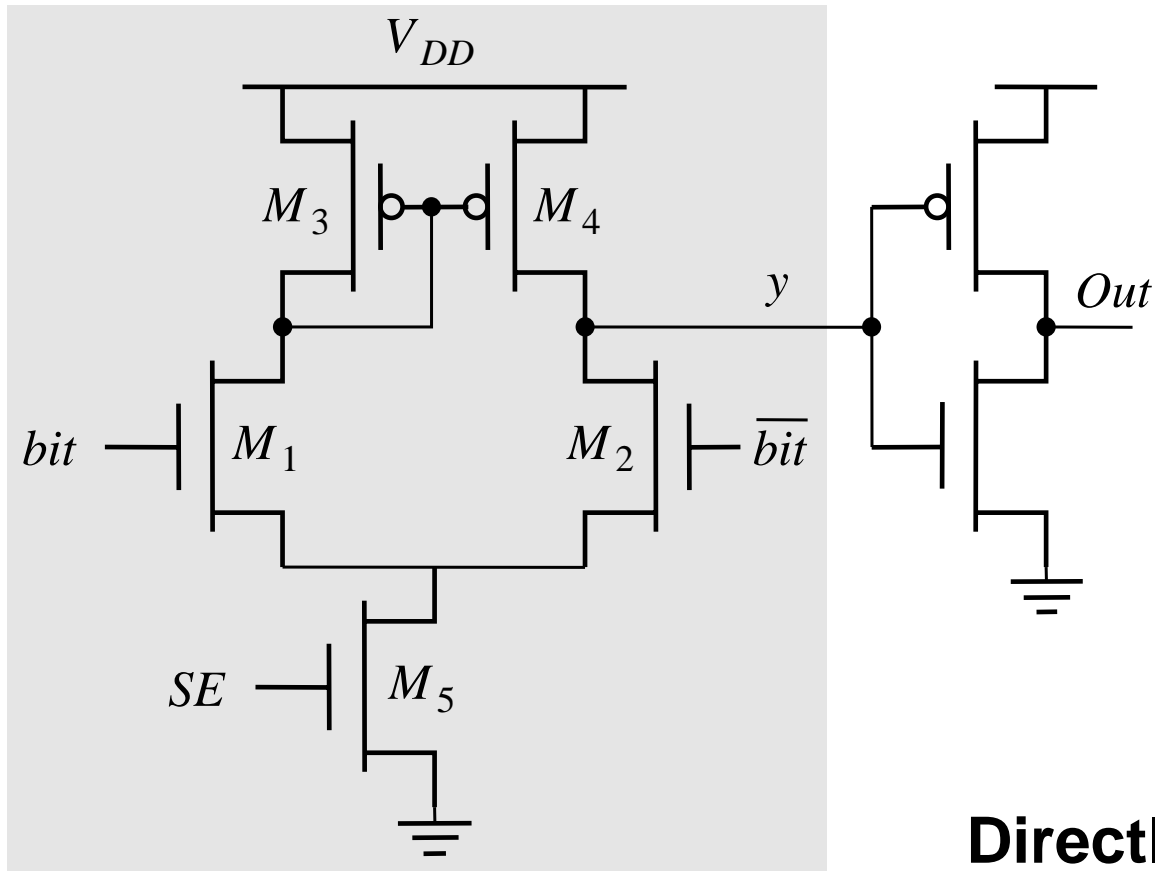


**Directly applicable to  
SRAMs**

# Differential Sensing – SRAM

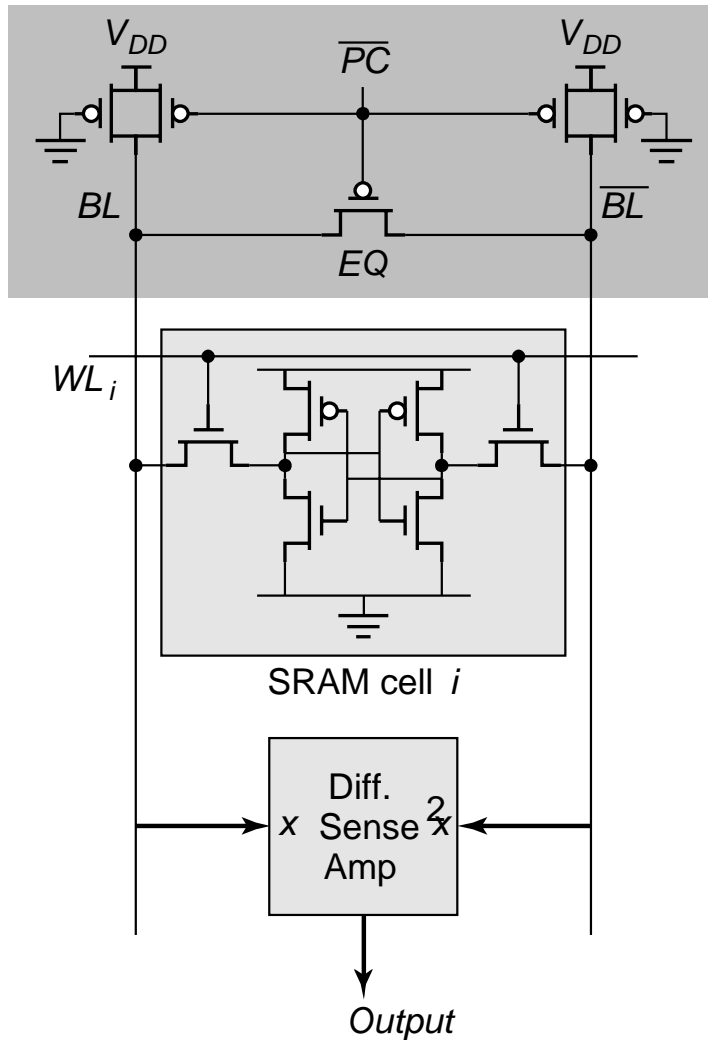


(a) SRAM sensing scheme

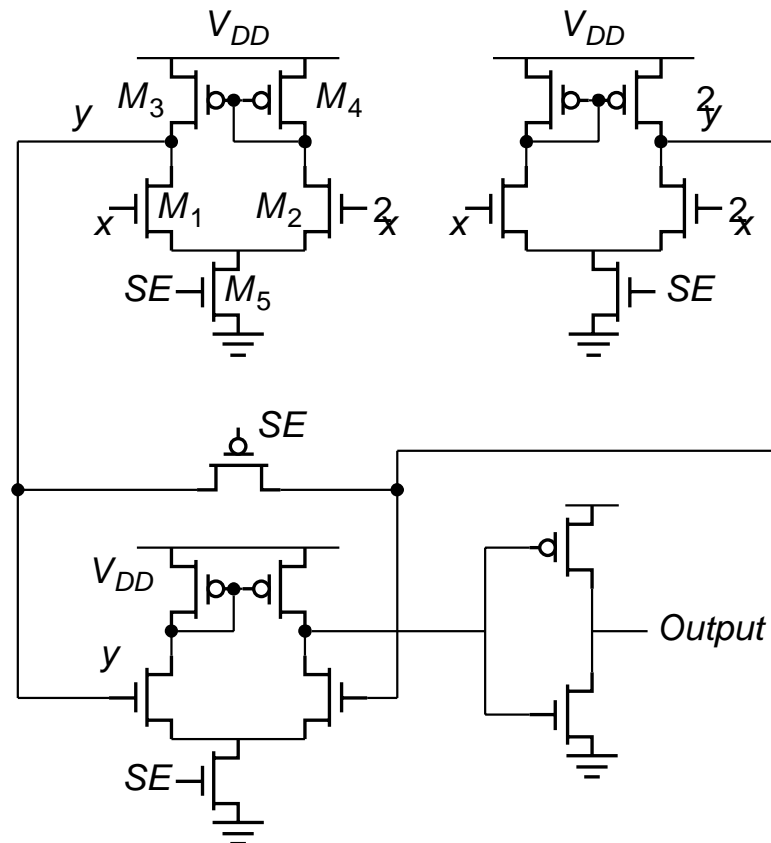

(b) two stage differential amplifier

# Latch-Based Sense Amplifier (DRAM)

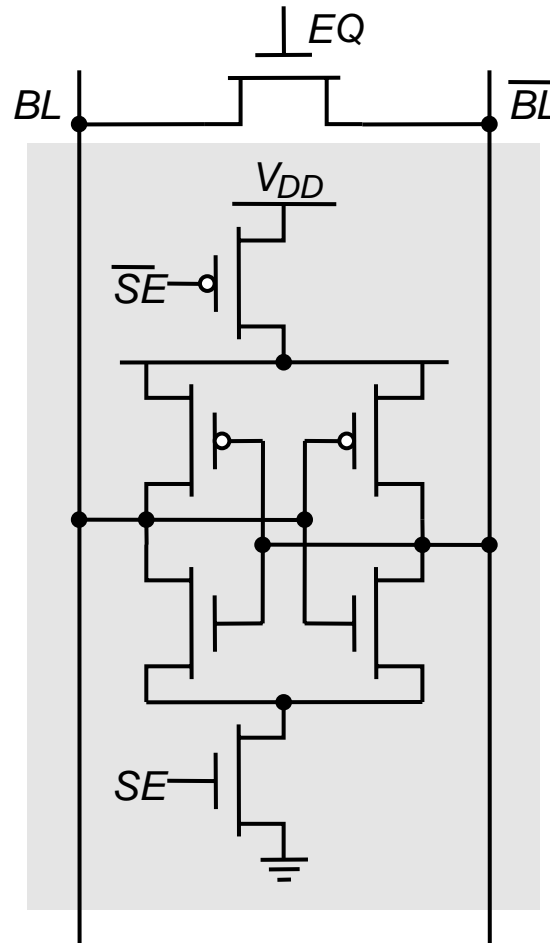


## Initialized in its meta-stable point with EQ

Once adequate voltage gap created, sense amp enabled with SE  
Positive feedback quickly forces output to a stable operating point.
 
# Reliability and Yield

- Semiconductor memories trade off noise-margin for density and performance



Highly Sensitive to Noise (Crosstalk, Supply Noise)

- High Density and Large Die size cause Yield Problems


$$Y = 100 \frac{\text{Number of Good Chips on Wafer}}{\text{Number of Chips on Wafer}}$$

$$Y = \left[ \frac{1 - e^{-AD}}{AD} \right]^2$$


**Increase Yield using Error Correction and Redundancy**




# Sensing Parameters in DRAM

 

# Noise Sources in 1T DRam

 


# Alpha-particles (or Neutrons)

 


**1 Particle ~ 1 Million Carriers**

# Yield

 

Yield curves at different stages of process maturity  
(from [Veendrick92])

# Redundancy

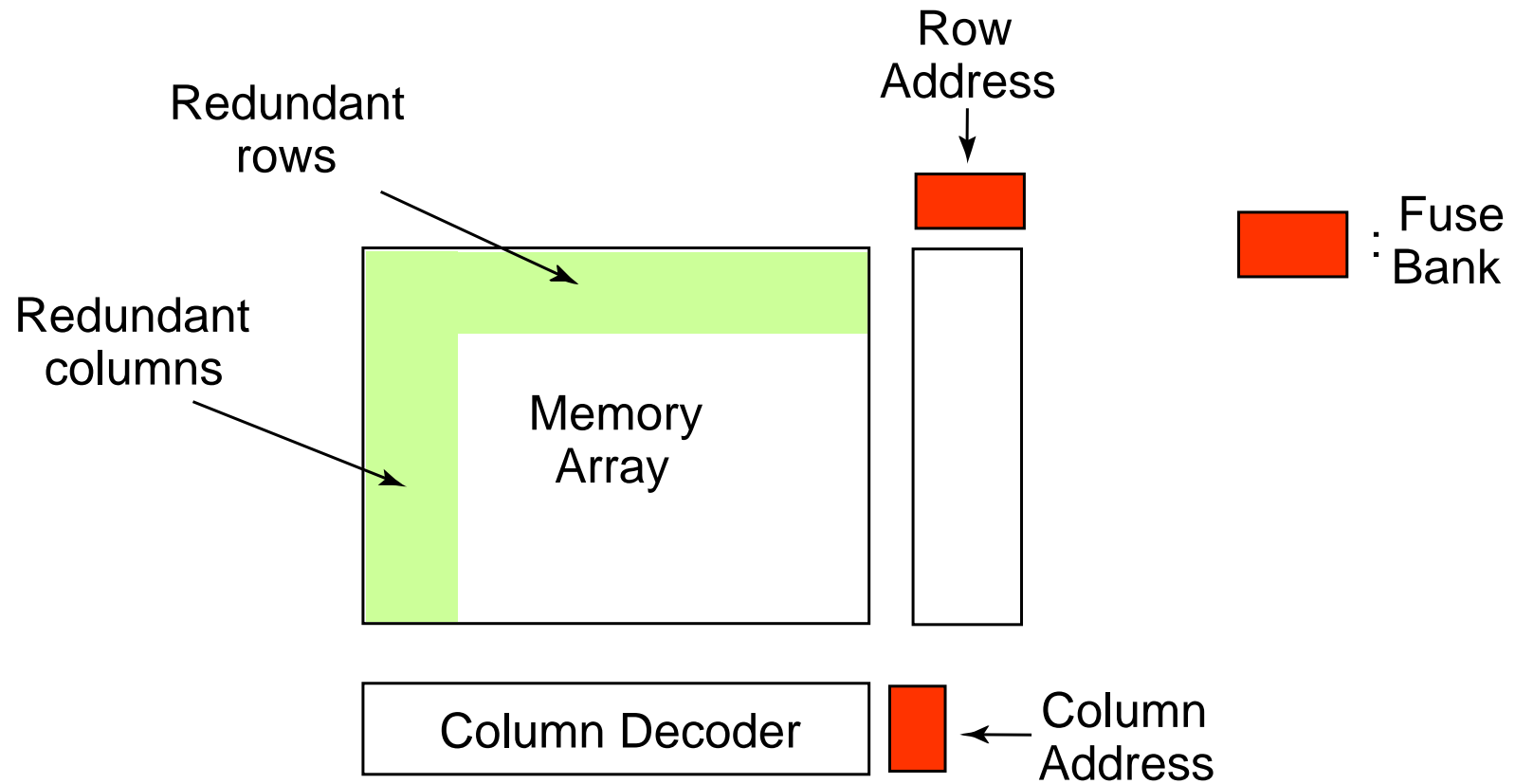

# Error-Correcting Codes

## Example: Hamming Codes

$P_1 P_2 B_3 P_4 B_5 B_6 B_7$

*with*

$$P_1 \oplus B_3 \oplus B_5 \oplus B_7 = 0$$

$$P_2 \oplus B_3 \oplus B_6 \oplus B_7 = 0$$

$$P_4 \oplus B_5 \oplus B_6 \oplus B_7 = 0$$


*e.g. B3 Wrong*

1

1 = 3

0

# Redundancy and Error Correction

 

# Case Studies

- ❑ Programmable Logic Array
- ❑ SRAM
- ❑ Flash Memory



# ***PLA versus ROM***

- ❑ **Programmable Logic Array**  
structured approach to random logic  
“two level logic implementation”  
NOR-NOR (product of sums)  
NAND-NAND (sum of products)

**IDENTICAL TO ROM!**

- ❑ **Main difference**  
ROM: fully populated  
PLA: one element per minterm


**Note: Importance of PLA's has drastically reduced**

- 1. slow**
- 2. better software techniques (multi-level logic synthesis)**


***But ...***

# Programmable Logic Array


## Pseudo-NMOS PLA

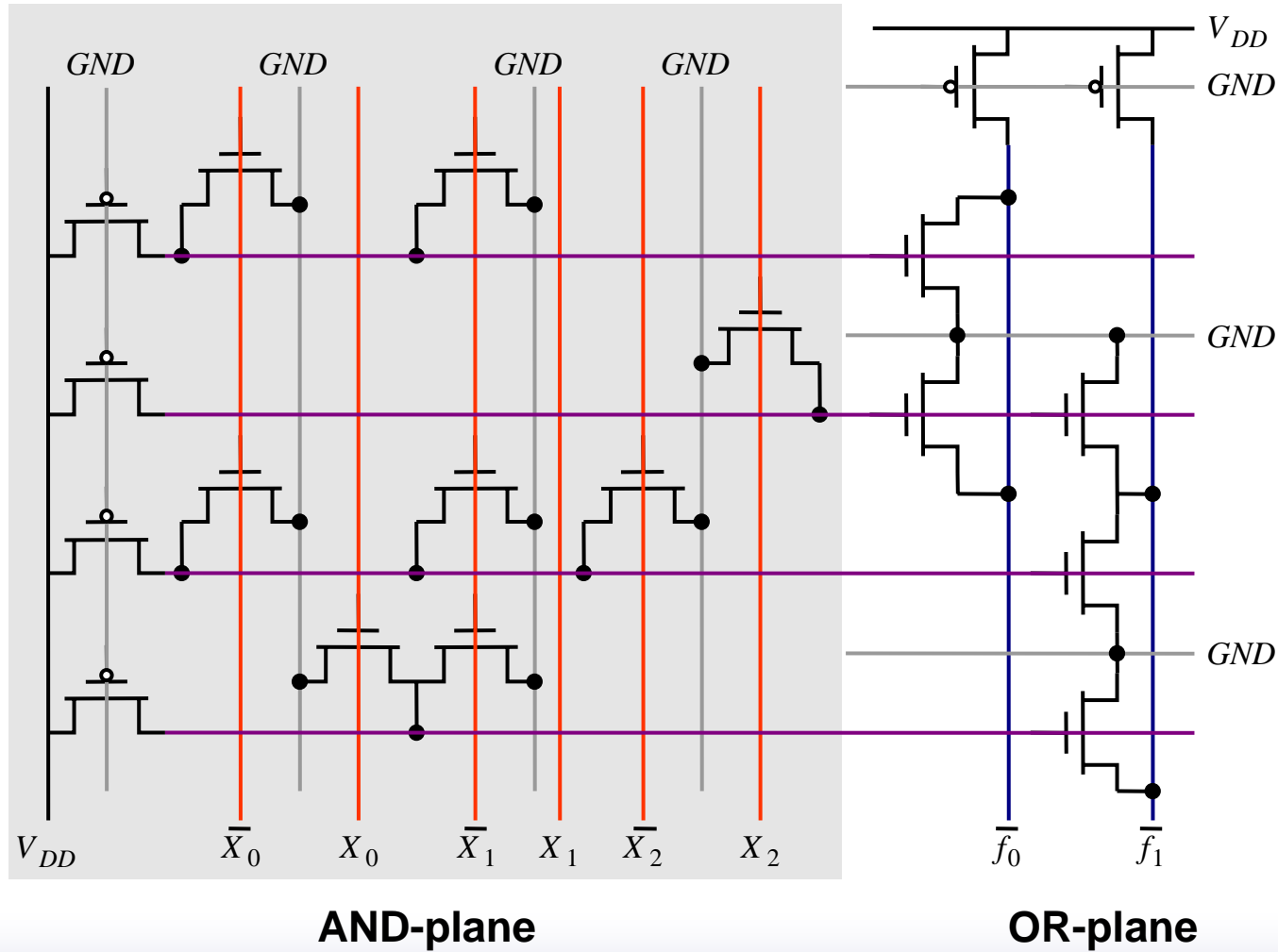


# Dynamic PLA

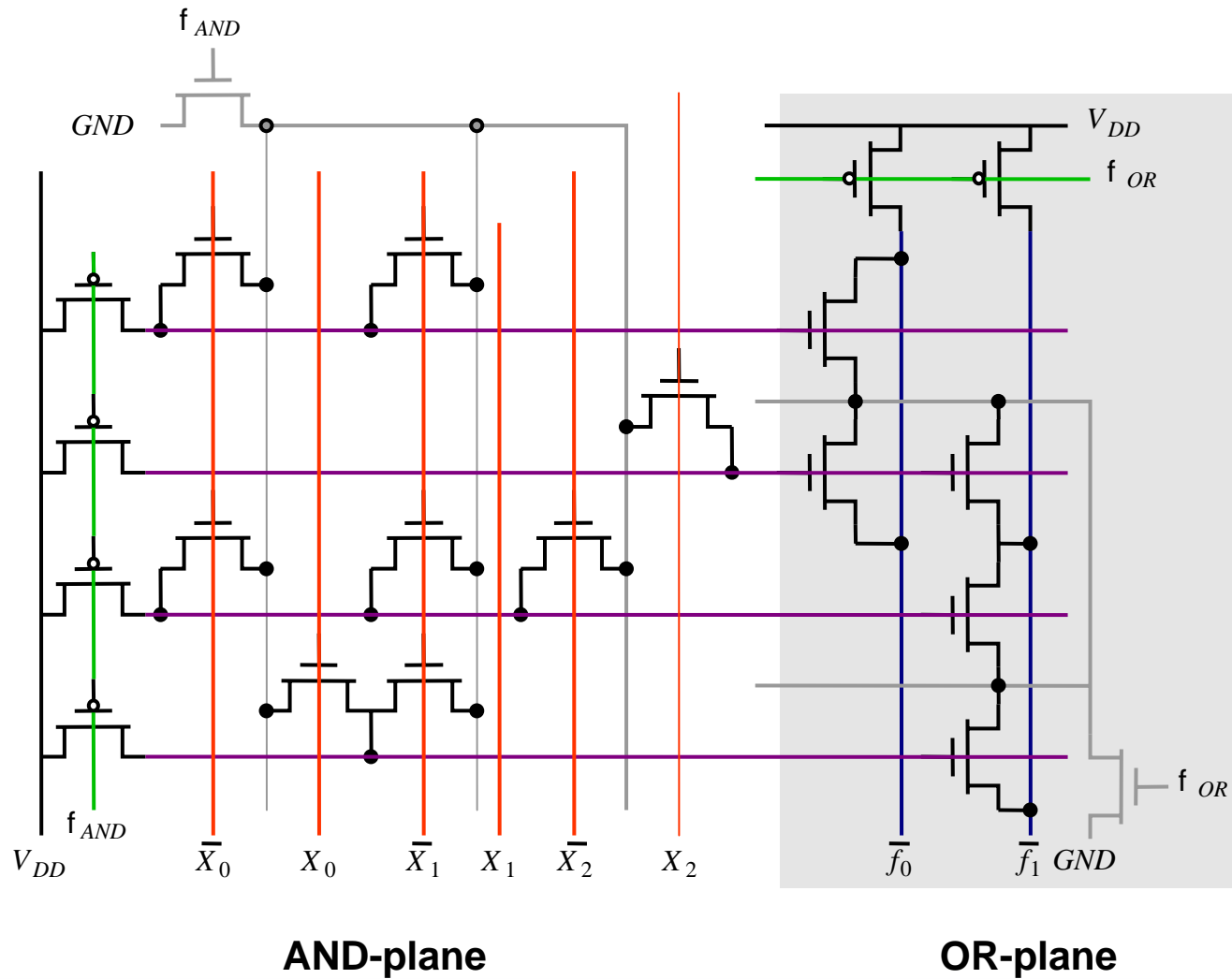
 
# Clock Signal Generation for self-timed dynamic PLA




(a) Clock signals

 


(b) Timing generation circuitry

# PLA Layout

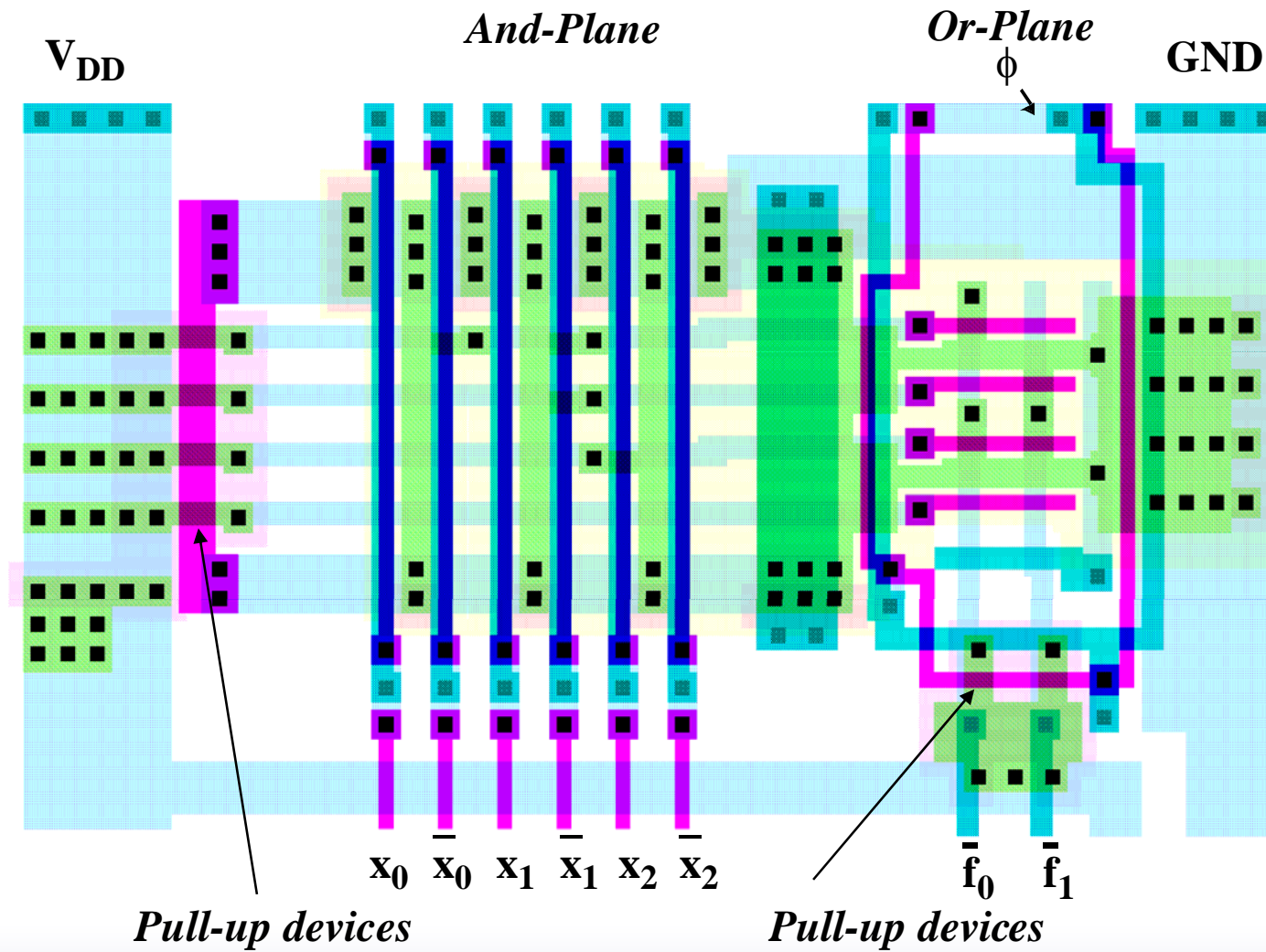


# 4 Mbit SRAM



## Hierarchical Word-line Architecture

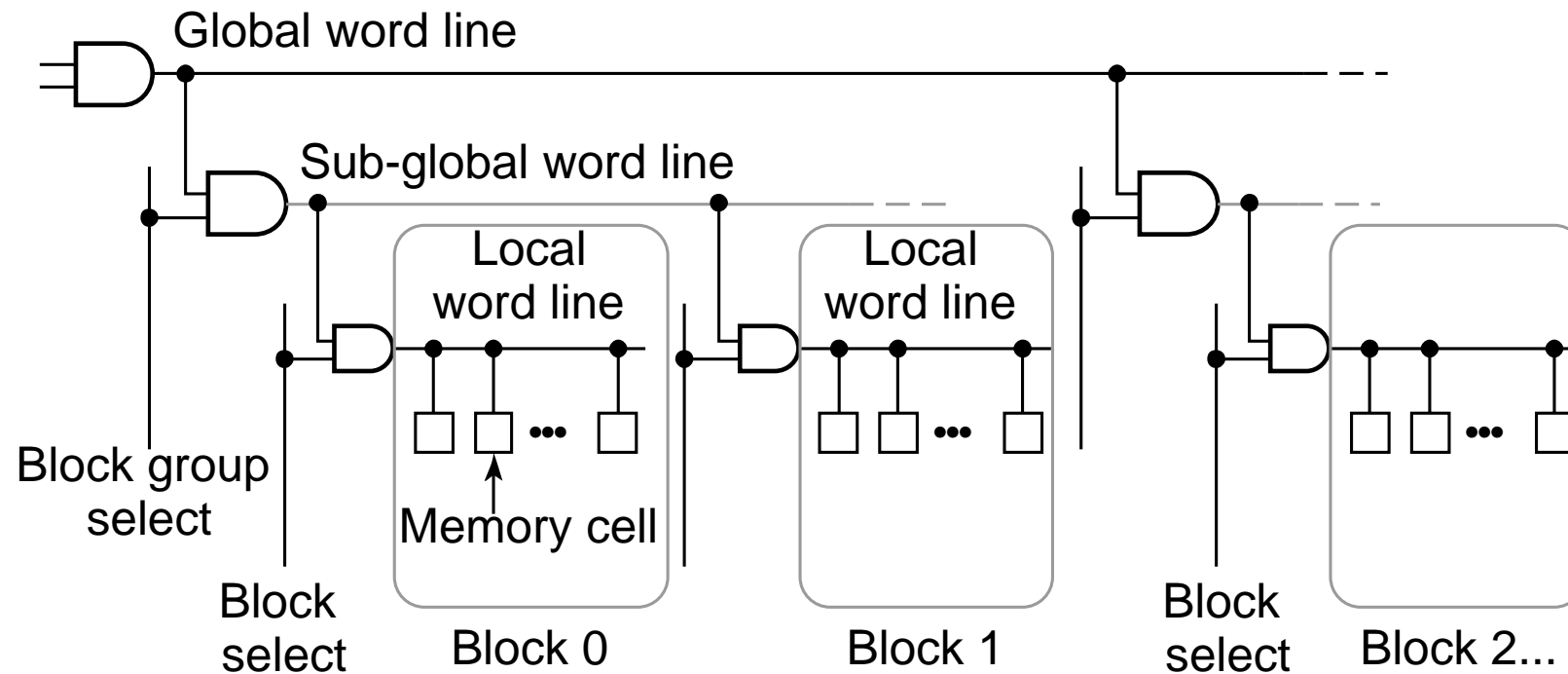

# Bit-line Circuitry

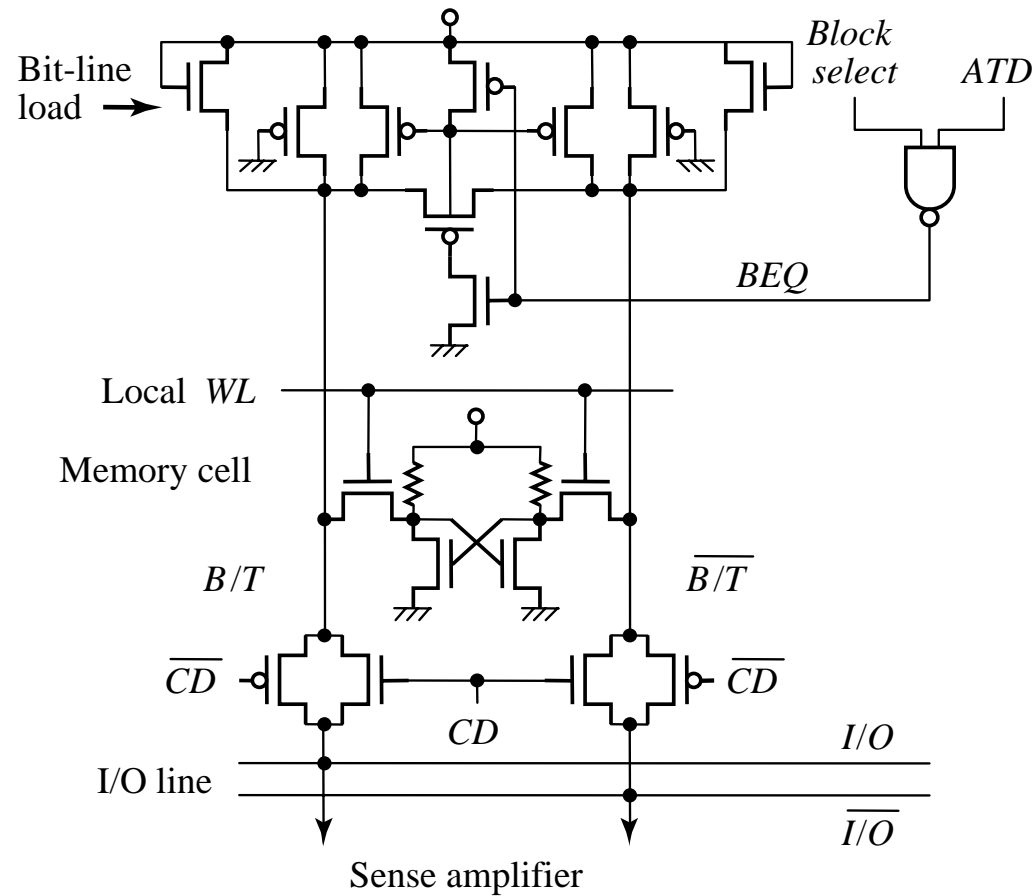


# Sense Amplifier (and Waveforms)

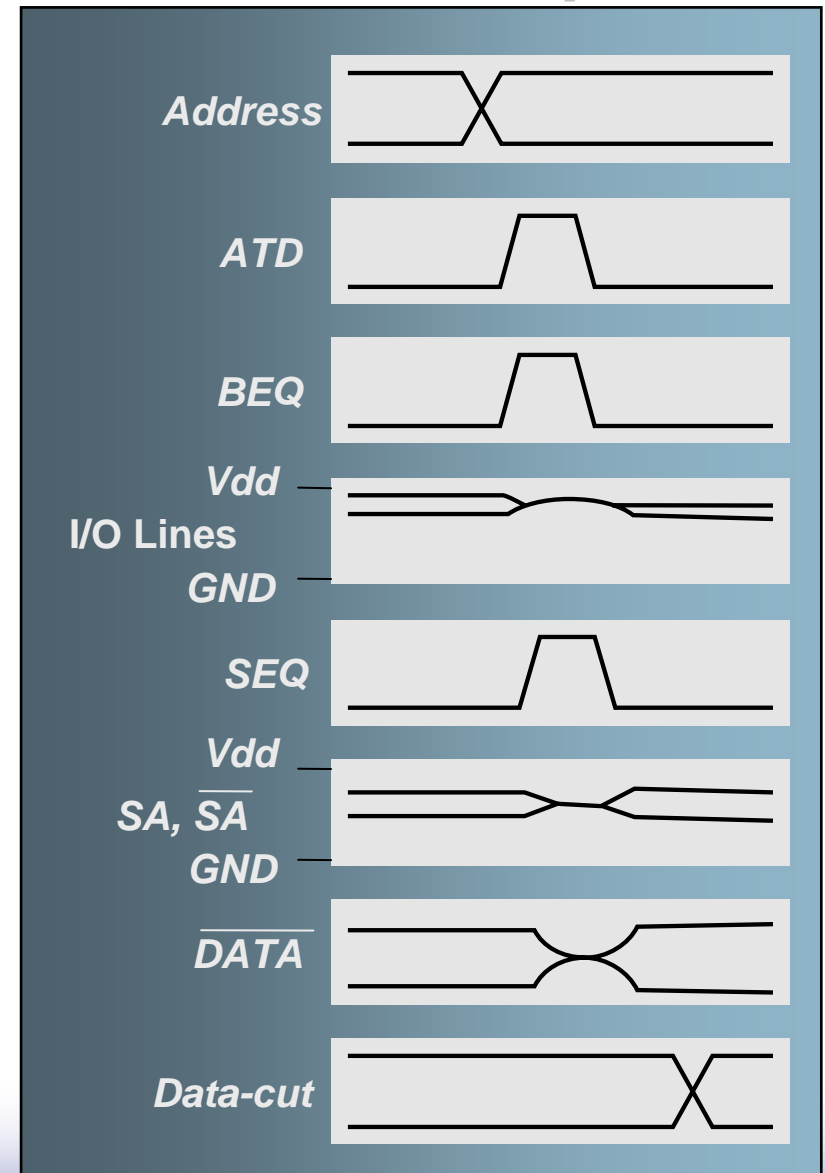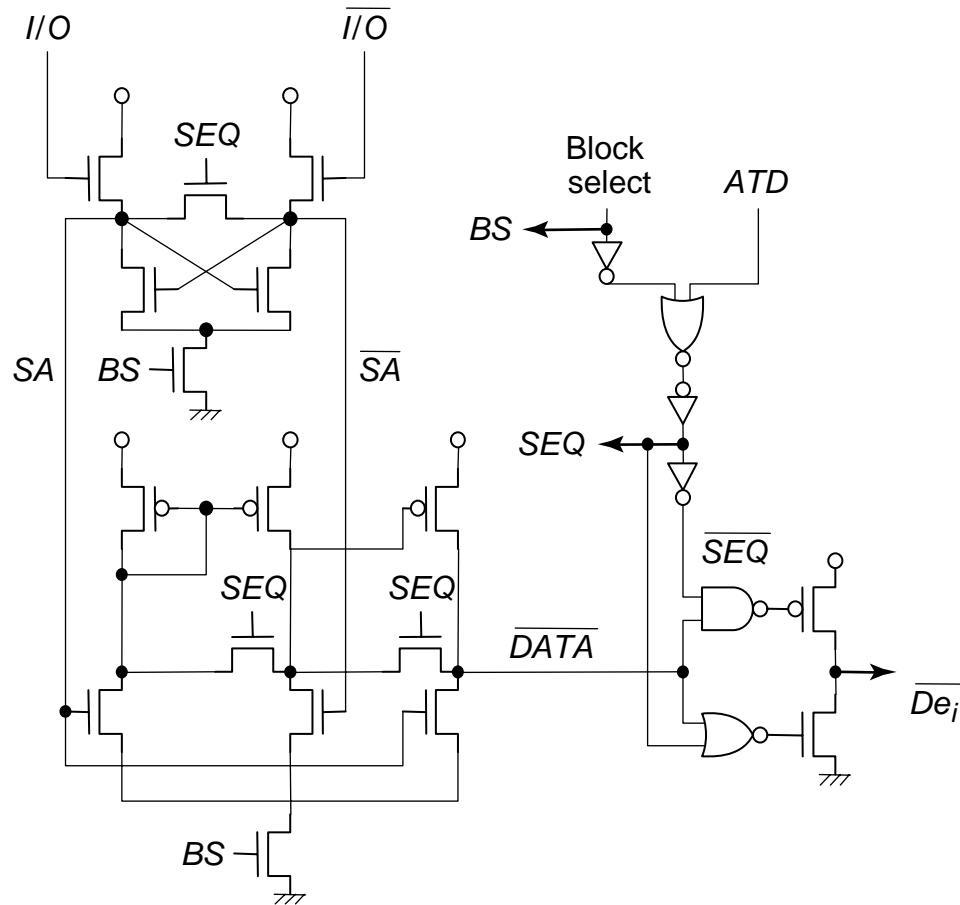


Memories




# 1 Gbit Flash Memory

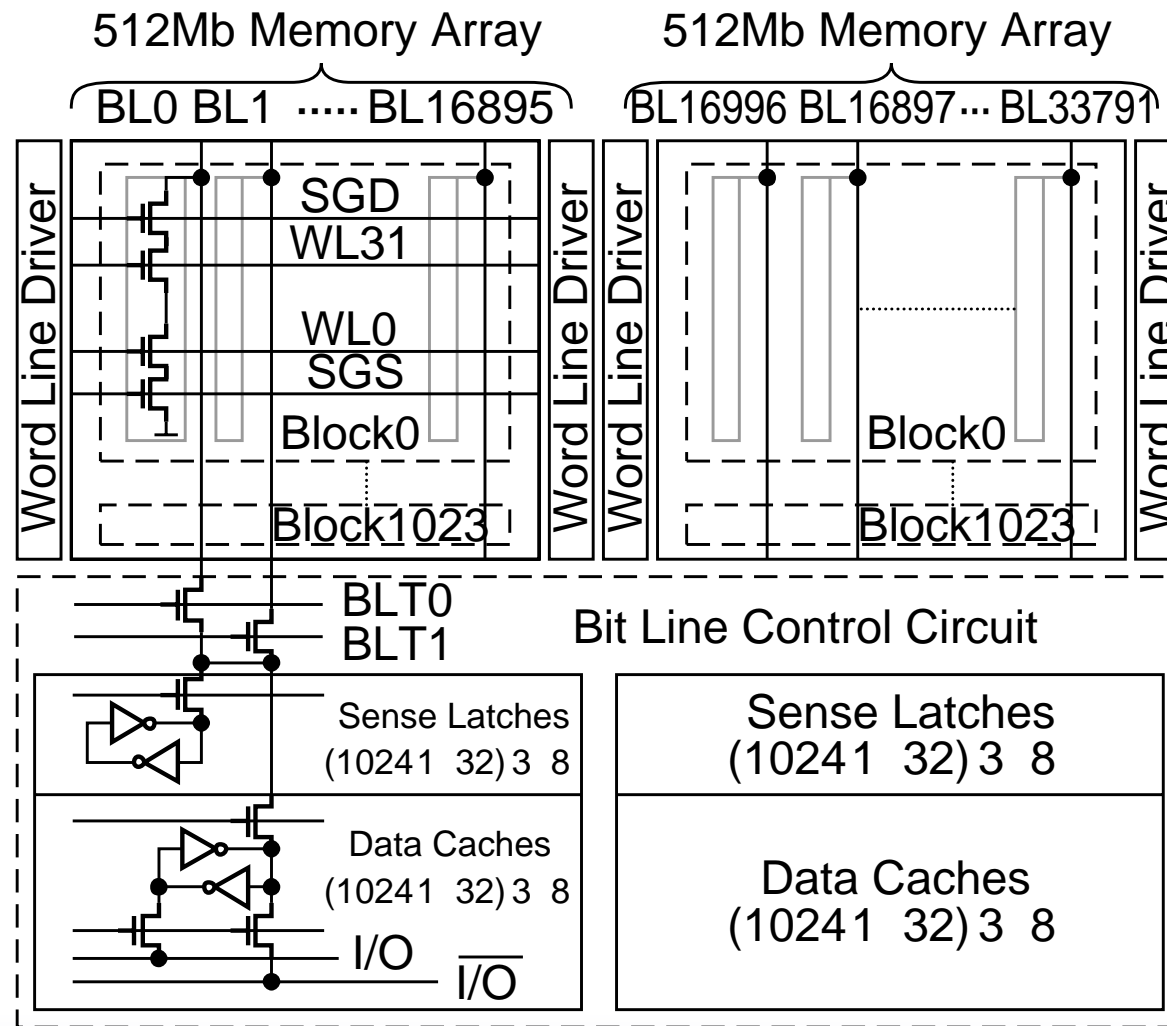

# Writing Flash Memory

 


**Evolution of thresholds**

 

**Final Distribution**

 
# *125mm<sup>2</sup> 1Gbit NAND Flash Memory*



# *125mm<sup>2</sup> 1Gbit NAND Flash Memory*


- ❑ **Technology**      0.13 $\mu$ m p-sub CMOS triple-well  
1poly, 1polycide, 1W, 2Al
- ❑ **Cell size**        0.077 $\mu$ m<sup>2</sup>
- ❑ **Chip size**        125.2mm<sup>2</sup>
- ❑ **Organization**    2112 x 8b x 64 page x 1k block
- ❑ **Power supply**    2.7V-3.6V
- ❑ **Cycle time**        50ns
- ❑ **Read time**        25 $\mu$ s
- ❑ **Program time**    200 $\mu$ s / page
- ❑ **Erase time**        2ms / block
 
# *Semiconductor Memory Trends (up to the 90's)*




Memory Size as a function of time: x 4 every three years


# Semiconductor Memory Trends (updated)

 

# *Trends in Memory Cell Area*

 

# Semiconductor Memory Trends

 

Technology feature size for different SRAM generations